

Roll No.															
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



School of Engineering

Mid - Term Examinations - Nov 2024

Semester: 5th

Date: 06/11/2024

Course Code: ECE3090

Time: 02.00pm to 03.30pm

Course Name: Digital System Design using VERILOG

Max Marks: 50

Program: B.Tech

Weightage: 25%

Instructions:

(i) Read all questions carefully and answer accordingly.

(ii) Do not write anything on the question paper other than roll number.

Part A

Answer ALL the Questions. Each question carries 2marks.

2Mx5Q=10M

1	VLSI is an implementation technology for electronic circuitry analogue or digital. List two popular VLSI platforms.	2	L1	C01
		Marks		
2	Design methodology and hierarchy decided the approach of solving the problems List two design methodology described in Verilog designing.	2	L1	C01
		Marks		
3	Demonstrate the levels of abstraction in VLSI using necessary diagram.	2	L1	C01
		Marks		
4	The basic unit of description in Verilog is the module, define module to design a X-Nor gate.	2	L1	C01
		Marks		
5	Explain the types of delays in Gate Level modeling of Verilog HDL with examples	2	L1	C02
		Marks		

Part B

Answer ALL Questions. Each question carries 10 marks.

4QX10M=40M

6	6a	Develop the Verilog HDL code for the SR Flip Flop using the logic diagram. Verify the developed code by using suitable test the input cases.	4 Marks	L3	C02
	6b	Utilize NAND gate to design the full adder circuit in gate level modeling of Verilog HDL code. Verify the developed code using the Test bench.	6 Marks	L3	C02

OR

- | | | | | | |
|----------|-----------|---|---------|----|-----|
| 7 | 7a | Model the 3 input NAND gate in transistor level to verify using the test bench | 4 Marks | L3 | CO2 |
| | 7b | Make use of 2 input EXOR gate transistor level circuit to verify its truth table. | 6 Marks | L3 | CO2 |

- | | | | | | |
|----------|-----------|--|---------|----|-----|
| 8 | 8a | Model the 8:3 Encoder using the Boolean expression and verify the test cases of the input. | 4 Marks | L3 | CO1 |
| | 8b | Develop the ALU circuit with using the conditional operator with its test bench. | 6 Marks | L3 | CO1 |

OR

- | | | | | | |
|----------|-----------|--|---------|----|-----|
| 9 | 9a | Develop the D-Flip Flop using the Dataflow modeling and simulate for all the test cases. | 4 Marks | L3 | CO1 |
| | 9b | Utilize NOR gate to design the full subtractor in dataflow modeling of Verilog HDL code. Verify the developed code using the Test bench. | 6 Marks | L3 | CO1 |

- | | | | | | |
|-----------|------------|--|---------|---|-----|
| 10 | 10a | In data flow modelling the keyword “assign” is used to define the output of a circuit. Draw the schematic corresponding to the output equation given below which uses conditional operators: | 6 Marks | L | CO1 |
|-----------|------------|--|---------|---|-----|

$$\text{assign } y = a ? (b ? i1 : i2) : (c ? i3 : i4)$$

- | | | | | | |
|--|------------|--|---------|---|-----|
| | 10b | Draw the schematic of the logic circuit described by the Verilog code below: | 4 Marks | L | CO2 |
|--|------------|--|---------|---|-----|


```

module example (a, b, c, y);
    input a, b, c;
    output y;
    assign y = ~a & b & ~c | ~a & ~b & ~c | a & ~b & ~c;
endmodule

```


OR

- | | | | | | |
|-----------|------------|--|---------|---|-----|
| 11 | 11a | A combinational circuit is a type of logic where each output depends only on its present input. For the combinational circuit shown below, write the Gate Level (Structural) Verilog description. Make sure that the internal and external signals are properly labeled. | 6 Marks | L | CO2 |
|-----------|------------|--|---------|---|-----|

 

11b Write the test bench for the circuit shown in 11(a) above. 4 Marks L CO2

 12 12a Switch level modeling in Verilog is a method used to describe digital circuits by focusing on the behavior of MOS transistors as electronic switches. For the circuit shown below, write the expression for the output 'Y' and write the Switch Level Verilog description. Make sure that the internal and external signals are properly labeled. 6 Marks L CO2



12b Write the test bench for the circuit shown in 12(a) above by considering only 4 combinations in which one of the transistors will have an input '1' and remaining three will have '0s'. e.g. ABCD = 1000. 4 Marks L CO2

OR

13 13a Construct the 3 input NOR gate in transistor level modelling. 4 Marks L CO

13b Develop the function $F = A + B(C + D)$ using the switch level modeling and verify using the test bench. 6 Marks L CO