

Roll No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



**PRESIDENCY
UNIVERSITY
BENGALURU**

School of Engineering

Mid - Term Examinations – Nov 2024

Semester: First

Date: 6-11-2024

Course Code: EEE1007

Time: 2:00pm – 3:30pm

Course Name: Basics of Electrical and Electronics Engineering

Max Marks: 50

Program: BE

Weightage: 25%

Instructions:

- (i) Read all questions carefully and answer accordingly.
- (ii) Do not write anything on the question paper other than roll number.

Part A

Answer ALL the Questions. Each question carries 2marks. 2Mx5Q=10M


1	Define active elements and passive elements of an electric circuit and give examples.	2 Marks	L	CO1
2	An alternating emf $E=110\sqrt{2} \sin 100t$ volt is applied to a capacitor of 2microF, the rms value of current in the circuit is ____	2 Marks	L	CO1
3	Energy band is a theoretical model describing the states of electrons, in materials, that can have values of energy only within certain specific ranges. Show the energy level diagram of insulators, Semi-conductors and conductor.	2 Marks	L	CO2
4	The single-phase circuits are electrical circuits that use a single alternating current (AC) waveform. In a pure capacitive circuit current ____ the voltage by an angle of ____.	2 Marks	L	CO2
5	Impurities are atoms that are added to a semiconductor to create different types of conductivity. Define donor and acceptor impurities with examples	2 Marks	L	CO2

Part B


Answer ALL Questions. Each question carries 10 marks. 4QX10M=40M

6	6a	A group of students are designing a simple filter using series combination of resistors and inductors. The circuit consists of a 10Ω resistor and a 200mH inductor connected in series with a AC voltage source. The rms voltage of the source is 12V, with a frequency of 50Hz. Calculate the power factor. Also indicate whether the voltage leads/lags the current in this circuit.	5Marks	L	CO1
---	----	--	--------	---	-----

6b	Three resistors $R_1=1.00\Omega$, $R_2=2.00\Omega$ and $R_3=2.00\Omega$ are connected in parallel. The parallel connection is attached to a $V=3.00V$ Voltage source. I. What is the equivalent resistance II. Find the current supplied by the source to the parallel circuit. III. Calculate the currents in each resistor and show that these add together to equal the current output of the source. IV. Calculate the power dissipated by each resistor. V. Find the power output of the source and show that it equals the total power dissipated by the resistors.	5Marks	L	CO1
Or				
7	7a An AC power source is a device that supplies AC power to various devices, such as lamps and household appliances. Describe the differences between real power, reactive power, and apparent power in an AC circuit. How is the power factor calculated?	5Marks	L	CO1
	7b Impedance is a measure of the opposition to electrical flow. What is the concept of impedance in an AC circuit? How does impedance differ from resistance? Explain the role of impedance in determining the phase relationship between voltage and current. Draw the vector diagram of RC Series Circuit.	5Marks	L	CO1
8	8a The relationship between the voltage across the junction and current through the circuit is known as the volt-ampere (V-I) characteristics of a PN junction diode. Explain V-I characteristics of PN junction diode with appropriate figures and list the applications of the diode.	5Marks	L	CO2
	8b The diode current equation describes the response of current through a diode to the voltage applied across it. Write the diode current equation and explain all the parameters in the diode equation.	5Marks	L	CO2
or				
9	9a A rectifier circuit is an electrical device that converts alternating current (AC) into direct current (DC). Draw the circuit diagram of full wave bridge rectifier with relevant input and output waveforms.	5Marks	L	CO2
	9b A filter circuit in a rectifier is used to transform a pulsating waveform into a constant DC waveform. Explain the working of shunt capacitor filter with relevant waveforms.	5Marks	L	CO2
10	10a Transformation allows us to convert one type of circuit connection into another type in order for us to easily analyse the circuit. Find the equivalent Delta circuit.	5Marks	L	CO1

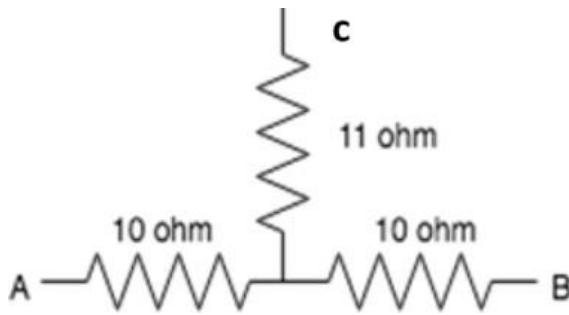


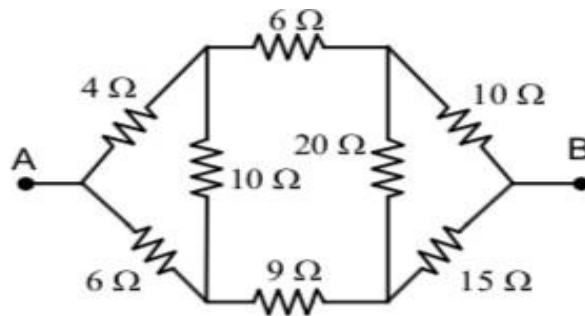- 10b** Star and Delta connections are two ways to connect three branches in an electrical network, forming either a Y shape or a triangle. Determine the equivalent resistance between terminals A and B 5Marks L CO1



or

- 11 11a** The combined effect of resistance R , inductive reactance X_L , and capacitive reactance X_C is defined to be impedance. A circuit consists of a resistance of $10\ \Omega$, an inductance of $16\ \text{mH}$ and a capacitance of $150\ \mu\text{F}$ in series. A supply of $100\ \text{V}$ at $50\ \text{Hz}$ is applied across the circuit. Find the power consumed by the circuit. Draw the vector diagram. 5Marks L CO1
- 11b** An RLC circuit is defined as a circuit where a resistor, inductor, and capacitor are connected in series across a voltage source, influencing the overall phase and magnitude of the circuit's impedance. A circuit consists of a resistance of $25\ \Omega$, and a capacitance of $100\ \mu\text{F}$ in series. A supply of $200\ \text{V}$ at $50\ \text{Hz}$ is applied across the circuit. Find the current, power factor and power consumed by the circuit. Draw the vector diagram. 5Marks L CO1
- 12 12a** In a semiconductor, the P-N junction is created by the method of doping. Explain the construction and working of PN junction diode in forward and reverse bias condition. 5Marks L CO2
- 12b** For the network shown in Fig., determine i_1 and i_2 . 5Marks L CO1

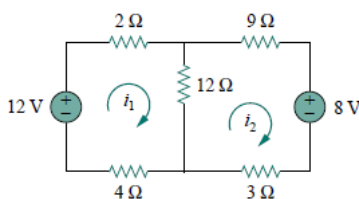

or

- 13 13a** State ohms law and its limitations. A resistance R is connected in series with a parallel circuit comprising two resistances of $12\ \Omega$ and 8Ω respectively. The total power dissipated in the circuit is 70 W when the applied voltage is 20V. Calculate R. 5Marks L C01
- 13b** A silicon diode working at a temperature of 30°C , the forward voltage applied across the diode is 0.6V. Determine its forward current, if the reverse saturation current is 20nA. 5Marks L C02