

| | | | | | | | | | | | | | | | | | | | |
|----------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| Roll No. | | | | | | | | | | | | | | | | | | | |
|----------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|



**PRESIDENCY
UNIVERSITY
BENGALURU**

School of Engineering

Mid - Term Examinations - November 2024

Semester: VII

Date: 05/11/2024

Course Code: ECE3050

Time: 02:00pm – 03:30pm

Course Name: DESIGN FOR TESTABILITY

Max Marks: 50

Program: B. TECH

Weightage: 25%

Instructions:

(i) Read all questions carefully and answer accordingly.

(ii) Do not write anything on the question paper other than roll number.

Part A

Answer ALL the Questions. Each question carries 2marks.

5QX2M=10M

- | | | | | |
|---|--|---------|----|-----|
| 1 | What are the different types of fault classes? | 2 Marks | L1 | CO1 |
| 2 | What are the DRCs that can result in low test coverage? | 2 Marks | L1 | CO2 |
| 3 | To quantify of the ease of testing two terms are commonly used in DFT i.e controllable and Observable. Define what is controllability and Observability? | 2 Marks | L1 | CO1 |
| 4 | Define the following terms. I) Defect ii) Fault | 2 Marks | L1 | CO1 |
| 5 | What is the significance of Lock up latch in digital design testing? | 2 Marks | L1 | CO2 |

Part B


Answer ALL Questions. Each question carries 10 marks.

4QX10M=40M


- | | | | | |
|---|--|---------|----|-----|
| 6 | 6a. VLSI testing is important to designers, product engineers, test engineers, managers, manufacturers, and end-users. Discuss Testing during VLSI Lifecycle? | 5 Marks | L2 | CO1 |
| | 6b. A VLSI design can be described at different levels of abstraction. Discuss different levels of abstraction in vlsi development process | 5 Marks | L2 | CO1 |

OR

 
- 7a. Find the test vector to be generated to detect stuck at 0 faults at net 'd' in the given circuit. **5 Marks L2 C01**



 - 7 **7b.** Find the test vector to be generated to detect faults at the input(A,B) and output(F) pf the OR gate which are stuck at 0 and 1 in the given circuit. **5 Marks L2 C01**




 - 8** Design truth tables for the fault-free circuit and the faulty circuits for all possible single stuck-at faults. **10Marks L3 C01**



OR

 - 9** Design truth tables for the fault-free circuit and the faulty circuits for all possible single stuck-at faults. **10Marks L3 C01**



- 10a.** In VLSI engineering a common fault after stuck at fault model is a bridging fault. Discuss the different types of bridging faults with an example. **5 Marks L3 CO2**
- 10**
- 10b.** IDDQ testing is a method for testing CMOS integrated circuits for the presence of manufacturing faults. Discuss Quiescent Drain Current testing(IDDQ) **5 Marks L3 CO2**
- 11a.** At the switch level, a transistor can be stuck-open or stuck-short, also referred to as stuck-off or stuck-on, respectively. Discuss Stuck-Open Fault Model with an example. **5 Marks L2 CO2**
- 11**
- 11b.** At the switch level, a transistor can be stuck-open or stuck-short, also referred to as stuck-off or stuck-on, respectively. Discuss Stuck-Short Fault Model with an example. **5 Marks L2 CO2**
- 12** Scan cell design is the most widely used structured DFT methodology. Explain about Edge triggered Muxed D Scan Cell design and test operation with suitable diagrams and waveforms? **10Marks L2 CO2**
- OR**
- 13** Within the field of electronics Level-sensitive scan design (LSSD) is part of an integrated circuit manufacturing test process. With neat diagram discuss the LSSD full scan design using double latch. **10Marks L2 CO2**