

Part C [Problem Solving Questions]

Answer both the Questions. Each Question carries ten marks. (2Qx10M=20M)

5. The switching characteristics of power BJT shown in Fig.1. The parameters are $V_{CC}=200V$, $V_{CE(sat)}=2V$, $I_{CEO}=2.5mA$, $I_{C(sat)}=80A$, $V_{BE(sat)}=2.5V$, $I_B=8A$, $t_d=0.4\mu s$, $t_r=0.9\mu s$, $t_s=5\mu s$, $t_f=3.2\mu s$, duty cycle (δ)=50% and switching frequency (f) is 10KHz. Sketch the instantaneous power curve due to collector current and determine average power loss (P_{AVIC}) due to collector current?

(C.O.NO.1) [Application]

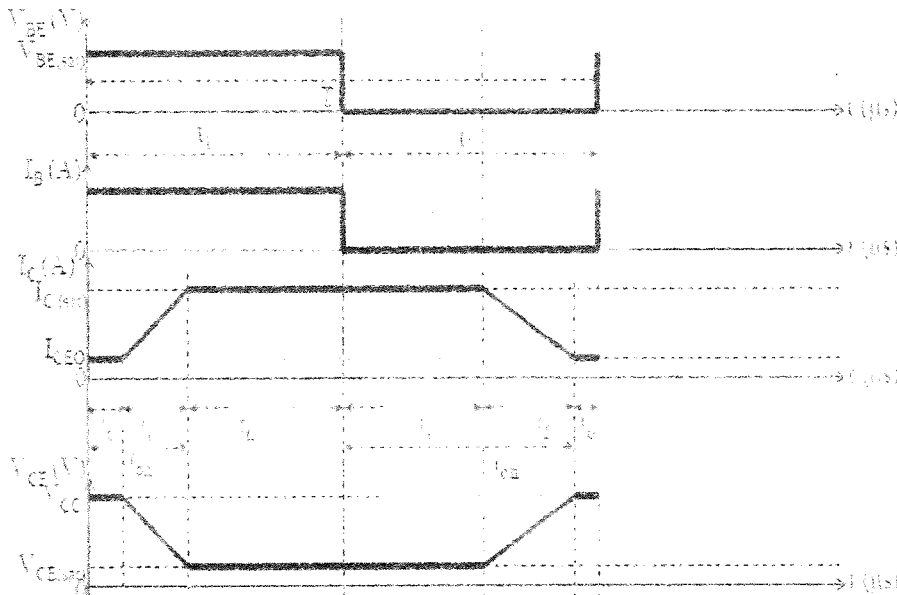


Fig. 1.

6. The power BJT circuit shown in Fig. 2. is specified to have β in the range 10 to 45, the load resistance $R_C=10\Omega$, $V_{CC}=200V$, $V_{BB}=10V$. If $V_{CE(sat)}=1V$ and $V_{BE(sat)}=1.5V$. Determine R_B that results in saturation with an ODF of 6?

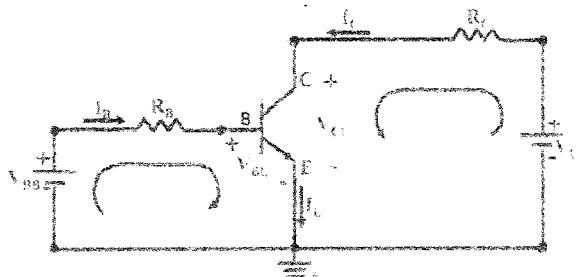


Fig. 2.

(C.O.NO.1) [Application]



SCHOOL OF ENGINEERING

SET A

Semester: V

Date: 01-10-2019

Course Code: ECE 302

Time: 2.30-3.30 PM

Course Name: Power Electronics

Max Marks: 40

Branch & Sem: ECE & V

Weightage: 20%

Extract of question distribution [outcome wise & level wise]

| Q.NO | C.O.NO | Unit/Module Number/Unit /Module Title | Memory recall type [Marks allotted] Bloom's Levels | | Thought provoking type [Marks allotted] Bloom's Levels | | Problem Solving type [Marks allotted] | | | Total Marks |
|------|--------|---|--|----|--|----|--|--|--|-------------|
| | | | K | L2 | C | L2 | A | | | |
| 1 | 1 | Module1/ Introduction, Power BJT and SCR | 04 | L2 | | | | | | 04 |
| 2 | 1 | Module1/ Introduction, Power BJT and SCR | 04 | L2 | | | | | | 04 |
| 3 | 1 | Module1/ Introduction, Power BJT and SCR | | | 06 | L2 | | | | 06 |
| 4 | 1 | Module1/ Introduction, | | | 06 | L2 | | | | 06 |

| | | | | | | | | | | |
|---|----------------|---|--|----|--|----|--|----|----|----|
| | | Power BJT and SCR | | | | | | | | |
| 5 | 1 | Module1/ Introduction, Power BJT and SCR | | | | | | 10 | L2 | 10 |
| 6 | 1 | Module1/ Introduction, Power BJT and SCR | | | | | | 10 | L2 | 10 |
| | Total Marks | 40 | | 08 | | 12 | | 20 | | |

K =Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.

[I hereby certify that All the questions are set as per the above guide lines. DR. Sreenivasappa B V]

Reviewers' Comments

Everything o.k. except uneven distribution of time in part 'C' when compared to marks.

Annexure- II: Format of Answer Scheme



SCHOOL OF ENGINEERING

SOLUTION

Semester: V

Course Code: ECE 302

Course Name: Power Electronics

Branch & Sem: ECE & V

Date: 01-10-2019

Time: 2.30-3.30 PM

Max Marks: 40

Weightage: 20%

Part A

(2Q x 4M = 8 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|--|--------------------|--------------------------------------|
| 1 | <p>Power electronics is an application of solid state electronics for the control and conversion of electric energy.</p> <p>Advantages: High reliable, efficiency, low losses, compact</p> <p>Disadvantages: Introduces harmonics into the source as well as load, electromagnetic interference</p> | 02 01 01 | 02 min 02 min |
| 2 | SCR, Power BJT, MOSFET, GTO | Each 01 mark (04) | 02 min |

Part B

(2Q x 6M = 12 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|--|--------------------------------------|--------------------------------------|
| 3 | <p>If the rate of rise of forward voltage $\frac{dv_s}{dt}$ is high then resultant high charging current can turn-on the SCR even when gate voltage is zero. This can be avoided by using a Snubber circuit connected in parallel with the device as shown in Fig. 1.</p> <div style="text-align: center;"> </div> <p>Fig. 1.</p> <p>The Snubber circuit is a series combination of resistance R_s and capacitance C_s. When SCR is off C_s charges to a voltage</p> | 01+01+01 02 01 | 10 min |

| | | | |
|---|---|----------------|--------|
| | equal to V_s . When SCR is on Cs discharges through SCR and sends current equal to $\frac{V_s}{R_s}$. | | |
| 4 | When the input voltage is large and if it is not possible to block this voltage with one SCR, then it is essential to connect two or more SCRs in series. Due to variation in the leakage current in each SCR, the voltage blocking will not be equal by each SCR. To overcome this problem it is necessary to connect a resistor of value R parallel to each SCR | 02 02 02 | 10 min |

Part C

(2Q x 10M = 20 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|---|--|--------------------------------------|
| 5 | $f=10\text{KHz}$ $T=1/f=1/10\text{KHz}=100\mu\text{s}$, $t_1=\delta T=50\mu\text{s}=t_2$ <u>Power loss due to I_c</u> Power loss due to t_d (P_{td}): $P_{td} = 0.5(t_d/T)=0.002\text{W}$ Power loss due to t_r (P_{tr}): $P_{tr} = (2/3)4000(t_r/T)=24\text{W}$ Power loss due to t_n (P_{tn}): $P_{tn} = 160(t_n/T)=77.92\text{W}$, $t_n=t_1-(t_d+t_r)=50\mu\text{s}-(1.3\mu\text{s})=48.7\mu\text{s}$ Power loss due to t_s (P_{ts}): $P_{ts} = 160(t_s/T)=8\text{W}$ Power loss due to t_f (P_{tf}): $P_{tf} = (2/3)4000(t_f/T)=85.33\text{W}$ Power loss due to t_o (P_{to}): $P_{to} = 0.5(t_o/T)=0.209\text{W}$, $t_o=t_2-(t_s+t_f)=50\mu\text{s}-(8.2\mu\text{s})=41.8\mu\text{s}$ $P_{AVIC} = P_{td}+P_{tr}+P_{tn}+P_{ts}+P_{tf}+P_{to}=195.461\text{W}$ | 01 01 01 01 01 01 01 02 | 20 min |
| 6 | We have $R_B = \frac{V_{BB}-V_{BE(sat)}}{I_B}$ $= \frac{10-1.5}{I_B} = \frac{10-1.5}{I_B} = \frac{8.5}{11.94} = 0.7118\Omega$ $ODF = \frac{I_B}{I_{B(sat)}}$ From this $I_B = I_{B(sat)} \times ODF$ $I_B = 1.99 \times 6 = 11.94\text{A}$ | 02 02 02 02 02 | 12 min |



Roll No.

**PRESIDENCY UNIVERSITY
BENGALURU**

SCHOOL OF ENGINEERING

TEST 2

Sem & AY: Odd Sem 2019-20

Course Code: ECE 302

Course Name: POWER ELECTRONICS

Program & Sem: B.Tech.(ECE) & V

Date: 19.11.2019

Time: 2.30 PM to 3.30 PM

Max Marks: 40

Weightage: 20%

Instructions:

- (i) Read the question properly and answer accordingly.
- (ii) Question paper consists of 3 parts.
- (iii) Scientific and Non-programmable calculators are permitted.

Part A [Memory Recall Questions]

Answer both the Questions. Each Question carries four marks. (2Qx4M=8M)

1. What is AC voltage controller? Give the classification of AC voltage controllers?
[4M] (C.O.NO. 1) [Bloom's level-L2]
2. What is the difference between semiconverter and full converter?
[4M] (C.O.NO. 1) [Bloom's level-L2]

Part B [Thought Provoking Questions]

Answer both the Questions. Each Question carries six marks. (2Qx6M=12M)

3. A 1- Φ half wave AC voltage controller has a resistive load of $R=6\Omega$ and input voltage $V_s=230V$, $50Hz$. The thyristor switch is triggered at an angle of $\alpha=\pi/2$. Determine (i) RMS output voltage (ii) Input power factor (iii) Average input current?
[6M] (C.O.NO. 1) [Bloom's level-L2]
4. A 2kW heater is connected across a 1- Φ 230V,50Hz, supply through an SCR. If the delay angle $\alpha \cong \frac{\pi}{4}$. Calculate the power observed by the heater element?
[6M] (C.O.NO. 1) [Bloom's level-L2]

Part C [Problem Solving Questions]

Answer both the Questions. Each Question carries ten marks. (2Qx10M=20M)

5. The step down chopper has resistive load of $R = 10\Omega$, the dc input voltage $V_s = 200V$ and voltage across the chopper when it is ON $V_{ch} = 2V$. If the chopping frequency $f = 1kHz$ and duty cycle is 70% determine (i) Average output voltage (ii) RMS output voltage (iii) Chopper efficiency (iv) Effective input resistance (v) RMS value of the fundamental component of the output voltage? [10M] (C.O.NO. 1) [Bloom's level-L2]

6. A 1- Φ ON-OFF AC voltage controller has a resistive load of $R=10\Omega$ and input voltage $V_s=120V$, 50Hz. The thyristor switch is ON for 25 cycles and OFF for 75 cycles. Determine (i) RMS output voltage (ii) Input power factor (iii) Average current of thyristor (iv) RMS currents of thyristor? [10M] (C.O.NO. 1) [Bloom's level-L2]



SCHOOL OF ENGINEERING

Semester: V
Course Code: ECE 302
Course Name: Power Electronics
Branch & Sem: ECE & V

Date: 19-11-2019
Time: 2.30-3.30 PM
Max Marks: 40
Weightage: 20%

Extract of question distribution [outcome wise & level wise]

| Q.NO | C.O.NO | Unit/Module Number/Unit /Module Title | Memory recall type [Marks allotted] Bloom's Levels | | Thought provoking type [Marks allotted] Bloom's Levels | | | Problem Solving type [Marks allotted] | | | Total Marks | |
|------|--------|---|---|----|---|--|----|---|--|----|----------------|----|
| | | | K | | C | | | A | | | | |
| 1 | 2 | Module2/ AC voltage controllers | | 04 | L2 | | | | | | | 04 |
| 2 | 2 | Module2/ Controlled rectifiers | | 04 | L2 | | | | | | | 04 |
| 3 | 2 | Module2/ AC voltage controllers | | | | | 06 | L2 | | | | 06 |
| 4 | 2 | Module2/ Controlled rectifiers | | | | | 06 | L2 | | | | 06 |
| 5 | 3 | Module3/ DC choppers | | | | | | | | 10 | L2 | 10 |

| | | | | | | | | | | | |
|---|-------------|---------------------------------|--|----|--|--|----|--|----|----|----|
| 6 | 2 | Module2/ AC voltage controllers | | | | | | | 10 | L2 | 10 |
| | Total Marks | 40 | | 08 | | | 12 | | 20 | | |

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.

Remarks.

1. All the questions are set for C.O. 1 only
what about other C.O.s?
2. In Thought provoking questions more problems are given. It should provoke the thought rather than like mathematical problems.
3. All the questions are set for Bloom level 2 only.

Annexure- II: Format of Answer Scheme



SCHOOL OF ENGINEERING

SOLUTION

Semester: V

Course Code: ECE 302

Course Name: Power Electronics

Branch & Sem: ECE & V

Date: 19-11-2019

Time: 2.30-3.30 PM

Max Marks: 40

Weightage: 20%

Part A

(2Q x 4M = 8 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|--|-------------------|--------------------------------------|
| 1 | <p>AC voltage controllers (ACVC) are power electronic converters that convert fixed AC to variable AC without changing frequency.</p> <p>There are two types in ACVC (i) ON-OFF ACVC (Integral grade ACVC) (ii) Phase angle ACVC – (ii.a) 1-Φ ACVC (ii.a.1) Unidirectional ACVC (Half wave ACVC) (ii.a.2) Bidirectional ACVC (Full wave ACVC) (ii.b) 3-Φ ACVC (ii.b.1) Unidirectional ACVC (Half wave ACVC) (ii.b.2) Bidirectional ACVC (Full wave ACVC)</p> | 02 | 02 min |
| | | 02 | 02 min |
| 2 | <p>Semiconverter operates in first quadrant where output voltage and current are positive and hence output power is positive.</p> <p>Full converter operates in first and fourth quadrants. In first quadrant output voltage and current are positive and hence output power is positive and in fourth quadrant output current is positive but output voltage is negative, hence output power is negative</p> | 02 | 02 min |
| | | 02 | |

Part B

(2Q x 6M = 12 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|--|-------------------|--------------------------------------|
| 3 | <p>$V_m = \sqrt{2}V_s = 325V$</p> <p>(i) $V_{orms} = \frac{V_s}{\sqrt{2\pi}} \sqrt{2\pi - \alpha + \frac{\sin 2\alpha}{2}} = 199.18V$</p> <p>(ii) $PF = PF = \frac{V_{orms}}{V_s} = 0.86$</p> | 01 | 10 min |
| | | 02 | |
| | | 01 | |

| | | | |
|---|---|----------------------|--------|
| | (iii) $V_{odc} = \frac{V_m}{2\pi} (\cos \alpha - 1), I_{odc} = \frac{V_{odc}}{R} = -8.62A$ | 02 | |
| 4 | $V_m = \sqrt{2} \cdot 230 = 325V$ Heater resistance is $R = \frac{V_S}{I_o} = \frac{V_S}{\left(\frac{P_o}{V_S}\right)} = \frac{V_S^2}{P_o} = \frac{230^2}{2000} = 26.45\Omega$ The power absorbed by the heater is $P_h = \frac{V_{orms}^2}{R} = \frac{(154.94)^2}{26.45} = 907.65W$ Where $V_{orms} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}} = 154.94V$ | 01 02 01 02 | 10 min |

Part C

(2Q x 10M = 20 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|---|----------------------------------|--------------------------------------|
| 5 | <p>$k = 0.7$</p> <p>(i) $V_{odc} = k(V_s - V_{ch}) = 138.6V$</p> <p>(ii) $V_{orms} = \sqrt{k}(V_s - V_{ch}) = 165.65V$</p> <p>(iii) $P_L = \frac{k(V_s - V_{ch})^2}{R} = 2744.28W$ $P_S = \frac{V_s k(V_s - V_{ch})}{R} = 2772W$ $\eta = \frac{P_L}{P_S} = 0.99$</p> <p>(iv) $R_i = \frac{V_s}{I_s} = \frac{V_s}{I_{odc}} = \frac{V_s}{\frac{V_{odc}}{R}} = \frac{V_s R}{k(V_s - V_{ch})} = 14.43\Omega$</p> <p>(v) The compact trigonometric Fourier series expansion for the output voltage waveform is given by</p> $v_o(t) = \frac{a_o}{2} + \sum_{n=1}^{\infty} v_{on} \sin(n\omega t + \phi_n)$ <p>Where $v_{on} = \sqrt{\frac{a_n^2 + b_n^2}{2}}$ = RMS value of the nth harmonic component of the output voltage.</p> $a_o = \frac{2}{T} \int_0^T v_o(t) dt$ | 01 01 02 01 02 01 | 20 min |

$$a_n = \frac{2}{T} \int_0^T v_o(t) \cos(n\omega t) dt$$

$$b_n = \frac{2}{T} \int_0^T v_o(t) \sin(n\omega t) dt$$

To find out RMS value of the fundamental component of the output voltage put $n=1$ in v_{on}

$$v_{o1} = \sqrt{\frac{a_1^2 + b_1^2}{2}} = \sqrt{\frac{(-29.97)^2 + (41.25)^2}{2}} = \sqrt{1299.8817}$$

$$= 36.05V$$

02

6

$$V_m = \sqrt{2}V_s = 169.7V, k = \frac{m}{m+n} = \frac{25}{25+75} = 0.25$$

(i) $V_{orms} = V_s \sqrt{k} = 60V$

(ii) $PF = \sqrt{k} = 0.5$

(iii) $I_{AT1} = \frac{kV_m}{\pi R} = 1.35A$

(iv) $I_{RT1} = \frac{\sqrt{k}V_m}{2R} = 4.24A$

01+02

02

01

02

02

12 min



| | | | | | | | | | | | | | | | | | | | |
|---------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| Roll No | | | | | | | | | | | | | | | | | | | |
|---------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

**PRESIDENCY UNIVERSITY
BENGALURU**

SCHOOL OF ENGINEERING

END TERM FINAL EXAMINATION

Semester: Odd Sem. 2019 - 20

Course Code: ECE 302

Course Name: POWER ELECTRONICS

Program & Sem: B.Tech (ECE) & V (DE-II)

Date: 23 December 2019

Time: 9.30 AM to 12.30 PM

Max Marks: 80

Weightage: 40%

Instructions:

- (i) Read the all questions carefully and answer accordingly.
- (ii) Question paper consists of 3 parts.
- (iii) Scientific and Non-programmable calculators are permitted.

Part A [Memory Recall Questions]

Answer all the Questions. Each Question carries 2 marks.

(10Qx2M=20M)

1. What are the applications of power electronics? (C.O.No.1) [Knowledge]
2. Mention various types of power converters? (C.O.No.1) [Knowledge]
3. What is the role of Snubber circuit in SCR? (C.O.No.1) [Knowledge]
4. What is inverter? (C.O.No.4) [Knowledge]
5. What is the range of output voltage in step-up chopper? (C.O.No.3) [Knowledge]
6. Classify control rectifiers? (C.O.No.2) [Knowledge]
7. What is the advantage of single phase full converter over semiconverter? (C.O.No.2) [Knowledge]
8. Write the output voltage equation for 1- Φ half bridge inverter? (C.O.No.4) [Knowledge]
9. Specify the reverse blocking voltage across each device in half bridge inverter? (C.O.No.4) [Knowledge]
10. Mention the applications of AC voltage controller? (C.O.No.2) [Knowledge]

Part B [Thought Provoking Questions]

Answer all the Questions. Each Question carries 6 marks.

(5Qx6M=30M)

11. If two bulbs of 100 W and 150 W are connected in series across a 230V AC power supply. Specify which bulb glow brighter and why? (C.O.No.2) [Comprehension]

12. Explain how 1- Φ full bridge inverter can be used as step down chopper?
(C.O.No.4) [Comprehension]
13. How do you generate two pulses per half cycle in single pulse width modulation?
(C.O.No.4) [Comprehension]
14. Explain how power flow can be controlled in both direction in chopper?
(C.O.No.3) [Knowledge]
15. In power electronics, explain how low power circuit is isolated from high power circuit?
(C.O.No.1) [Knowledge]

Part C [Problem Solving Questions]

Answer all the Questions. Each Question carries 10 marks. (3Qx10M=30M)

16. A step up chopper has an input voltage of 220V and an output voltage of 600V. if the non-conducting time of the chopper is $100\mu s$. Calculate the pulse width. In case the pulse width is divided into two equal parts for constant frequency operation. Find the new output voltage.
(C.O.No.3) [Comprehension]
17. The half wave controlled rectifier has a purely resistive load of R and the delay angle is $\alpha = \pi/3$. Determine (i) η (ii) FF (iii) RF (iv) TUF (v) PIV (C.O.No.1) [Comprehension]
18. The 1- Φ half bridge inverter has a resistive load of 10Ω and the DC input voltage is 24V. Calculate (i) RMS output voltage (ii) Fundamental component of the output voltage (iii) First five harmonics of the output voltage (iv) Fundamental power consumed by the load (v) RMS power consumed by the load. (C.O.No.4) [Comprehension]



SCHOOL OF ENGINEERING

END TERM FINAL EXAMINATION

Extract of question distribution [outcome wise & level wise]

| Q.NO | C.O.NO (% age of CO) | Unit/Module Number/Unit /Module Title | Memory recall type | Thought provoking type | Problem Solving type | Total Marks |
|------|----------------------------|---|------------------------------------|------------------------------------|-------------------------|----------------|
| | | | [Marks allotted] Bloom's Levels | [Marks allotted] Bloom's Levels | [Marks allotted] A | |
| | | | K | C | A | |
| 1 | 1 | 1 | 2 | | | 2 |
| 2 | 1 | 1 | 2 | | | 2 |
| 3 | 1 | 1 | 2 | | | 2 |
| 4 | 4 | 4 | 2 | | | 2 |
| 5 | 3 | 3 | 2 | | | 2 |
| 6 | 2 | 2 | 2 | | | 2 |
| 7 | 2 | 2 | 2 | | | 2 |
| 8 | 3 | 3 | 2 | | | 2 |
| 9 | 4 | 4 | 2 | | | 2 |
| 10 | 2 | 2 | 2 | | | 2 |
| 11 | 1 | 1 | | 6 | | 6 |
| 12 | 4 | 4 | | 6 | | 6 |
| 13 | 4 | 4 | | 6 | | 6 |
| 14 | 2 | 2 | 6 | | | 6 |
| 15 | 1 | 1 | 6 | | | 6 |
| 16 | 3 | 3 | | 10 | | 10 |
| 17 | 1 | 1 | | 10 | | 10 |

| | | | | | | |
|----|-------------|---|----|----|--|----|
| 18 | 4 | 4 | | 10 | | 10 |
| | Total Marks | | 32 | 48 | | 80 |

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.

I hereby certify that all the questions are set as per the above guidelines.

Faculty Signature:

Reviewer Comment: Dr. LEVY. M

- (1) Faculty Not signed
- (2) Distribution of Marks. —,
- (3) Thought provoking questions — ?
- (4) Step Marks — ?
- (5) Question numbers 1-18 — ?



SCHOOL OF ENGINEERING

SOLUTION

Semester: Odd Sem. 2019-20
 Course Code: ECE 302
 Course Name: POWER ELECTRONICS
 Program & Sem: B.TECH & V

Date: 23.12.2019
 Time: 3 HRS
 Max Marks: 80
 Weightage: 40%

Part A

(10Q x 2M = 20Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|--|-------------------|--------------------------------------|
| 1 | <p style="text-align: center;">Power Electronics</p> <ul style="list-style-type: none"> Aerospace: Aircraft power system, Space shuttle power supplies, Satellite power supplies Commercial: Advertising, heating, air-conditioning power supplies, computer, office equipment, elevators, light dimmer, uninterruptible power supplies, central refrigeration Industrial: Industrial furnaces, blowers and fans, pumps and compressors, industrial lasers, transformer tap changers, rolling mills, textile mills, cement mills, welding Transportation: Traction control of electric vehicles, electric locomotives, trolley buses, subways, automotive electronics Residential: Air conditioning, cooking, lighting, refrigerators, electric-door openers, dryers, fans, personal computers, vacuum cleaners, washing machine, food mixers | 2 | 3min |
| 2 | <p style="text-align: center;">Uncontrolled/ Controlled rectifiers</p> <p style="text-align: center;">AC voltage controllers/ Cycloconverters Static switches DC choppers</p> <p style="text-align: center;">Inverters</p> | 2 | 3min |
| 3 | <p>This can be avoided by using a Snubber circuit connected in parallel with the device as shown in Figure</p> <div style="display: flex; justify-content: space-around; align-items: center;"> </div> | 2 | 3min |

| | | | |
|----|--|---|------|
| | The Snubber circuit is a series combination of resistance R_S and capacitance C_S . When SCR is off C_S charges to a voltage equal to V_S . When SCR is on C_S discharges through SCR and sends current equal to $\frac{V_S}{R_S}$. | | |
| 4 | Inverter is a power electronic converter that converts fixed DC input voltage to a symmetrical AC output voltage of desired magnitude and frequency. Inverters are also known as DC-AC converters. | 2 | 2min |
| 5 | $V_o = V_s / (1-K)$, if $K=0$ $V_o = V_s$ If $K=1$ $V_o = \square$ | 2 | 4min |
| 6 | <p style="text-align: center;">Controlled Rectifiers</p> | 2 | 4min |
| 7 | Power flow is in both the direction i.e. from source to load and load to source | 2 | 2min |
| 8 | $V_o(\text{average}) = 0$ and $V_o(\text{rms}) = V_s/2$ | 2 | 1min |
| 9 | reverse blocking voltage across each device in half bridge inverter is $V_s/2$ | 2 | 2min |
| 10 | These are used in (i) Transformer tap changer (ii) Induction heating (iii) Light intensity control (iv) Speed control of induction motor. | 2 | 1min |


Part B

(5Q x 6M = 30 Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|---|-------------------|--------------------------------------|
| 11 | $P_{100W} = V^2 / R_{100W}$, $R_{100W} = 529 \Omega$ and $R_{150W} = 352.66 \Omega$ $I = 230 / (881.66) = 0.26$ Power loss due to 100 W and 150 W $P_{100W} = I^2 R_{100W} = 36W$ $P_{150W} = I^2 R_{150W} = 23.83W$ Hence 100 W bulb glow brighter than 150 W bulb | 2 2 1 1 | 15min |
| 12 | <p>In the above figure to operate single phase full bridge inverter turn-on both Q1 and Q2 at a time and</p> | 4 2 | 15min |

turn-off both Q3 and Q4 and vary the duty cycle

13

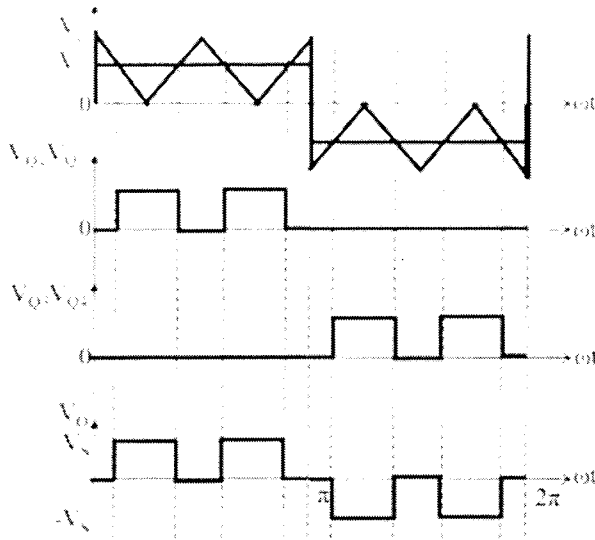

2

1


1

2

15min

14

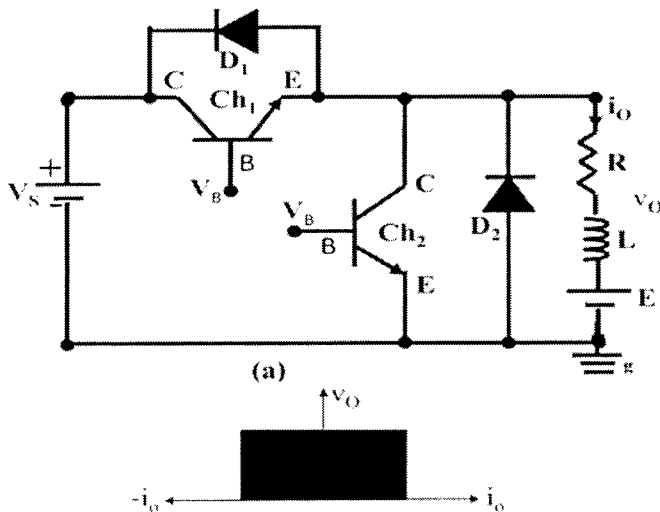Power flow in both direction in chopper is done using class C chopper



1

3

2

20min

15


In power electronics the control circuit works at lower voltages and currents (low power) and the power converter works at higher voltages and currents (high power). The control circuits are easily damaged if exposed to high power. Hence, isolation is necessary between control circuit and power converter to protect control circuit from high power.

There are two ways of isolation (i) Pulse transformers (ii) Optocouplers

2

1

15min

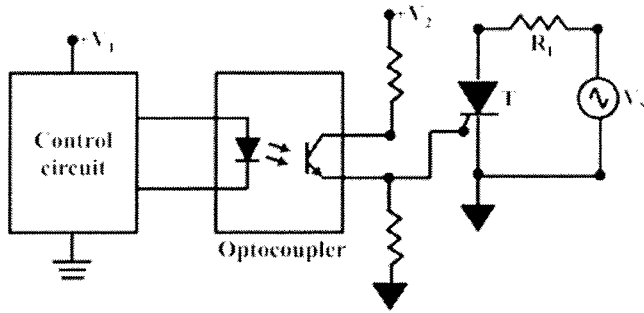

3

Part C

(3Q x 10M = 30Marks)

| Q No | Solution | Scheme of Marking | Max. Time required for each Question |
|------|---|---|--------------------------------------|
| 16 | <p>The relation between input and output voltage for step up chopper is</p> $V_o = V_s \left[\frac{1}{1-k} \right]$ $k = 0.63$ <p>But $k = \frac{t_1}{T}$ The pulse width of the o/p voltage is $t_1 =$</p> $kT = kt_1 + kt_2 = \frac{kt_2}{1-k} = \frac{0.63 \times 100 \times 10^{-6}}{1-0.63} = 170 \mu s$ $T = t_1 + t_2 = 170 \mu s + 100 \mu s = 270 \mu s$ <p>If the pulse width is divided into two equal parts</p> $t'_1 = \frac{t_1}{2} = 85 \mu s$ <p>For constant frequency chopper T remains constant and hence $T = t'_1 + t'_2$</p> $t'_2 = T - t'_1 = 270 \mu s - 85 \mu s = 185 \mu s$ <p>New duty cycle $k' = \frac{t'_1}{T} = \frac{85 \mu s}{270 \mu s} = 0.3148$</p> <p>The new output voltage is</p> $V'_o = V_s \left[\frac{1}{1-k'} \right] = 220 \left[\frac{1}{1-0.3148} \right] = 321.07V$ | <p>02</p> <p>02</p> <p>02</p> <p>02</p> <p>02</p> | <p>20min</p> |
| 17 | <p>(i) $\eta = \frac{P_{odc}}{P_{oac}} = \frac{P_{odc}}{P_{orms}} = \left(\frac{V_{odc}}{V_{orms}} \right)^2 = \left(\frac{\frac{V_m}{2\pi}(1+\cos\alpha)}{\frac{V_m}{2\sqrt{\pi}}\sqrt{\pi-\alpha+\frac{\sin 2\alpha}{2}}} \right)^2 =$</p> | <p>02</p> | <p>20min</p> |

| | | | |
|----|---|----|-------|
| | 0.2833 | 02 | |
| | (ii) $FF = \frac{V_{orms}}{V_{odc}} = 1.87$ | 02 | |
| | (iii) $RF = 1.21$ | 02 | |
| | (i) $TUF = 0.1432$ | 02 | |
| | (ii) $PIV = V_m$ | 02 | |
| 18 | $V_S = 24V, R = 10\Omega$ | | 20min |
| | (i) $V_{orms} = \frac{V_S}{2} = 12V$ | 01 | |
| | (ii) $v_{o1} = 0.45V_S = 10.8V$ | 01 | |
| | (iii) We have $v_{on} = \frac{1}{\sqrt{2}} \frac{2V_S}{n\pi}$ $v_{o3} = 3.6V,$ $v_{o5} = 2.16V, v_{o7} = 1.54V, v_{o9} = 1.2V,$ $v_{o11} = 0.98V$ | 06 | |
| | (iv) $P_{o1} = \frac{v_{o1}^2}{R} = 11.664W$ | 01 | |
| | (v) $P_{orms} = \frac{V_{orms}^2}{R} = 14.4W$ | 01 | |

