



**PRESIDENCY UNIVERSITY  
BENGALURU  
SCHOOL OF ENGINEERING**

Roll No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**TEST 1**

**Sem & AY:** Odd Sem. 2019-20

**Date:** 01.10.2019

**Course Code:** ECE 215

**Time:** 1:00PM to 2:00PM

**Course Name:** VLSI DESIGN

**Max Marks:** 40

**Program & Sem:** B.Tech. (ECE) & VII

**Weightage:** 20%

**Instructions:**

- i. Answer all the Questions.

**Part A [Memory Recall Questions]**

**Answer all the Questions. Each question carries two marks. (5Qx2M=10M)**

1. What are the different levels of Design Description?
2. Define Data Flow style of modeling?
3. What is HDL? Name some HDLs?
4. Write the operator symbols for Bitwise logical operators?
5. Write the syntax for 2 types of Tristate Inverters?

[Q.No.1 to 5] (C.O.NO.1) [Knowledge]

**Part B [Thought Provoking Questions]**

**Answer all the Questions. Each question carries five marks. (3Qx5M=15M)**

6. What is contention? Demonstrate with a Verilog Module?
7. Write a Verilog Module and Test Bench for half adder in Structural style?
8. Write a Verilog Module and Test bench for 2X1 MUX using Ternary Operator?

[Q.No.6 to 8] (C.O.NO.1) [Comprehension]

**Part C [Problem Solving Questions]**

**Answer the Question. The Question carries fifteen marks. (1Qx15M=15M)**

9. Explain Design flow with a neat sketch? Write a Verilog module and Test Bench for UPCOUNTER in behavioral style? (C.O.NO.1) [Comprehension]





**SCHOOL OF-ENGINEERING**

Date: 01-10-2019

Time: 1 hour

Max Marks: 40

Weightage: 20%

Semester: 7

Course Code: ECE 215

Course Name: VLSI Design

**Extract of question distribution [outcome wise & level wise]**

Q.NO	C.O.NO	Unit/Module Number/Unit /Module Title	Memory recall type			Thought provoking type			Problem Solving type	Total Marks
			[Marks allotted]	Bloom's Levels		[Marks allotted]	Bloom's Levels			
			K			C			A	
1-5	CO 1	Module 1	10							10
1-3	CO 1	Module 1				5	5	5		15
1	CO 1	Module 1				10			15	15
	<b>Total Marks</b>									40

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.


[I hereby certify that All the questions [are set as per the above guide lines. Mr. Vijaya Krishna ]

Reviewers' Comments

- ① The BP has been set exactly for 60 minutes. At least 05 minutes should be given for reading the Q.s.
- ② For Part 'c', expected solution seems lengthy as per the marks assigned.



# Annexure- II: Format of Answer Scheme

 

SCHOOL OF ENGINEERING

SOLUTION

Date 01-10-2019

Semester: 7

Time: 1 hour

Course Code: ECE 215

Max Marks:40

Course Name: VLSI Design

Weightage 20%

## Part A

(5Q x 2M = 10 Marks)


Q No	Solution	Scheme of Marking	Max. Time required for each Question						
1	Structural, Dataflow, Behavioral	2	2						
2	Data Flow is defined as set of concurrent statements.	2	2						
3	Hardware Description Language, VHDL, and Verilog	2	2						
4	AND & OR   XOR ^ XNOR ~^	2	2						
5	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 25%; padding: 5px;">not a=0 (out = 1 control)</td> <td style="width: 25%; text-align: center; padding: 5px;"> </td> <td style="width: 50%; padding: 5px;">Out = complement of in control = 1 out = 0</td> </tr> <tr> <td style="padding: 5px;">not a=0 (out = 0 control)</td> <td style="text-align: center; padding: 5px;"> </td> <td style="padding: 5px;">Out = complement of in control = 0 out = 1</td> </tr> </table>	not a=0 (out = 1 control)		Out = complement of in control = 1 out = 0	not a=0 (out = 0 control)		Out = complement of in control = 0 out = 1	2	2
not a=0 (out = 1 control)		Out = complement of in control = 1 out = 0							
not a=0 (out = 0 control)		Out = complement of in control = 0 out = 1							

## Part B

(3Q x 5M = 15Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question
1	<p>If a wire takes two different values from different sources then contention arises. A single wire cannot hold two values at a time. To avoid contention nets are given with different strengths.</p> <p>Module contres(c,a,b):            Input a,b:            Output c:            buf (supply 1, pull0) g1(c,a,g2(c,b)).            endmodule</p>	2+2+1=5	5



 

2

3+2=5

5

Half adder



a	b	S	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Module

```

timescale 1ms/1ns;
module Ha(s,c,a,b);
output s,c;
input a,b;
xor x1(s,a,b);
and a1(c,a,b);
endmodule

```






```

timescale 1ms/1ns,
module tb1(),
wire s, c;
reg a, b;
#10 H1 (s, c, a, b);
initial begin
    a = 0, b = 0;
#2 a = 0, b = 1;
#3 a = 1, b = 0;
#4 a = 1, b = 1;
#10 $stop;
end.
endmodule.

```

3

2x1 MUX module

 

```

timescale 1ms/1ns;
module mux21 (z, a, b);

```

```

    output z;

```

```

    input a, b;

```

```

    assign z = (s == 0) ? a : b;

```

```

endmodule

```

3+2=5

5



```

module mux2_1_tb (
    wire z;
    reg s, a, b;
    mux2_1 m1 (z, a, b);
    initial begin
        s = 0; a = 0; b = 0;
        #2 s = 0; a = 0; b = 1;
        #4 s = 1; a = 1; b = 0;
        #10 $stop;
    end
endmodule

```



No	Question	Marks	Time required for each Question
1	<p><b>Design Flow:</b></p> <p>There are several steps in a VHDL-based design process, often called the design flow.</p>	10-3-2-15	35

Hierarchy/Block Diagram

The “front end” begins with figuring out the basic approach and building blocks at the block diagram level. Large logic designs, like software programs, are usually hierarchical, and VHDL gives us a good framework for defining modules and their interfaces, and filling in the details.

Coding:

The actual writing of VHDL code for modules, their interfaces, and their internal details. VHDL is a text-based language, in principle you can use any text editor for this part.

A specialized VHDL text editor include features like automatic highlighting of VHDL keywords, automatic indenting, built-in templates for frequently used program structures, and built-in syntax checking and one-click access to the compiler.

Compiler:

A VHDL compiler analyzes your code for syntax errors and also checks your code for compatibility with other modules on which it relies

It also creates the internal information that is needed for a simulator to process your design later. As in other programming endeavors, you probably shouldn't wait until the very end of coding to compile all of your code.

Doing a piece at a time can prevent you from proliferating syntax errors, inconsistent



### Simulator:

A VHDL simulator allows you to define and apply inputs to your design, and to observe its outputs, without ever having to build the physical circuit.

In small projects we would probably generate inputs and observe outputs manually. But for larger projects, VHDL gives you the ability to create "test benches" that automatically apply inputs and compare them with expected outputs.

There are two types of verification:

- 1) Functional Verification
- 2) Timing Verification

In functional verification, we study the circuit's logical operation independent of timing considerations: gate delays and other timing parameters are considered to be zero.

In timing verification, we study the circuit's operation including estimated delays, and we verify that the setup, hold, and other timing requirements for sequential devices like flip-flops are met. Functional verification is done before starting the back-end steps.

In back-end there are three basic steps:

- 1) Synthesis
- 2) Fitting/Place & Route
- 3) Timing Verification

### Synthesis:

The synthesis is converting the VHDL description into a set of primitives or components that can be assembled in the target technology.

For example, with PLDs or CPLDs, the synthesis tool may generate two-level sum-of-products equations. In the fitting step, a fitting tool or fitter maps the synthesized primitives or components onto available device resources.

### Place & Route:

For a PLD or CPLD, this may mean assigning equations to available AND-OR elements. For an ASIC, it may mean laying down individual gates in a pattern and finding ways to connect them within the physical constraints of the ASIC die. The "final" step is timing verification of the fitted circuit. Actual circuit delays due to wire lengths, electrical loading, and other factors can be calculated with reasonable precision.





```
module count_up(a, clk, N),
```

```
input clk;
```

```
input [3:0] N;
```

```
output [3:0] a;
```

```
reg [3:0] a;
```

```
initial a = 4'b0000;
```

```
always @ (negedge clk)
```

```
    a = (a == N) ? 4'b0000 : a + 1'b1;
```

```
endmodule
```

```
module test_count_up,
```

```
reg clk;
```

```
reg [3:0] N;
```

```
wire [3:0] a;
```

```
count_up ci(a, clk, N);
```

```
initial
```

```
begin
```

```
    clk = 0;
```

```
    N = 4'b1011;
```

```
end
```

```
always #12 clk = ~clk;
```

```
endmodule
```





Roll No.																				
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**PRESIDENCY UNIVERSITY  
BENGALURU  
SCHOOL OF ENGINEERING**

**TEST – 2**

**Sem & AY: Odd Sem 2019-20**

**Date: 19.11.2019**

**Course Code: ECE 215**

**Time: 1.00 PM to 2.00 PM**

**Course Name: VLSI DESIGN**

**Max Marks: 40**

**Program & Sem: Btech. (ECE) & VII Sem**

**Weightage: 20%**

**Instructions:**

- (i) Read Questions carefully and answer accordingly.
- (ii) Scientific and Non- programmable calculators are permitted.

**Part A [Memory Recall Questions]**

**Answer all the Questions. Each question carries two marks. (5Qx2M=10M)**

**(C.O.NO.2&3)[Knowledge]**

1. Define Moore's Law?
2. Write the Expression for Trans-conductance?
3. What is Lithography?
4. Which layers are used for forming PMOS transistor?
5. Draw the stick encoding for Implant and write its color?

**Part B [Thought Provoking Questions]**

**Answer all the Questions. Each question carries five marks. (3Qx5M=15M)**

**(C.O.NO.3)[Comprehension]**

6. Explain NMOS Inverter with circuit diagram?
7. Draw the Layout for 3 input NMOS NAND gate with color representation?
8. Explain Lambda based design rules for Wires and Transistors?

**Part C [Problem Solving Questions]**

**Answer the Question. The question carry fifteen marks. (1Qx15M=15M)**

9. Derive the Expression for  $I_{ds}$  (drain to source current) of MOS transistor in Non-Saturation and Saturation regions?  
**(C.O.NO.2)[Comprehension]**





**SCHOOL OF-ENGINEERING**

Semester: 7  
 Course Code: ECE 215  
 Course Name: VLSI Design

Date: 19-11-2019  
 Time: 1 hour  
 Max Marks: 40  
 Weightage: 20%

**Extract of question distribution [outcome wise & level wise]**

Q.NO	C.O.NO	Unit/Module Number/Unit /Module Title	Memory recall type			Thought provoking type			Problem Solving type			Total Marks
			[Marks allotted]	Bloom's Levels		[Marks allotted]	Bloom's Levels		[Marks allotted]	Bloom's Levels		
			K			C			A			
1-5	CO 2	Module 2	10									10
	CO 3	Module 3										
1-3	CO 3	Module 3				5	5	5				15
1	CO 2	Module 2							15			15
	Total Marks											40

Reviewer's Comments:

① Questions are well planned, however following observations I have:

- Thought provoking questions are replaced with explanation based questions

- Problem Solving Type question contains a derivation. Small portion of evaluation could have been included.

Pringh  
14/11/19

## Annexure- II: Format of Answer Scheme



### SCHOOL OF ENGINEERING

#### SOLUTION

Date: 19-11-2019

Time: 1 hour

Max Marks: 40

Weightage: 20%

Semester: 7


Course Code: ECE 215

Course Name: VLSI Design

#### Part A


(5Q x 2M = 10 Marks)


Time for reading question paper 5 Min

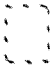Q No	Solution	Scheme of Marking	Max. Time required for each Question
1	The number of transistors doubled approximately every 18 months.	2	2
2	$g_m = \frac{\mu \epsilon_{ins} \epsilon_0}{D} \frac{W}{L} (V_{gs} - V_t)$	2	2
3	It is used to pattern specific shapes of a thin layer on a rigid substrate for fabricating electrical devices. These devices are the result of direct and monolithic integration of several layers on a wafer.	2	2
4	Poly silicon and P diffusion	2	2
5	 Yellow	2	2

Part B

(3Q x 5M = 15Marks)

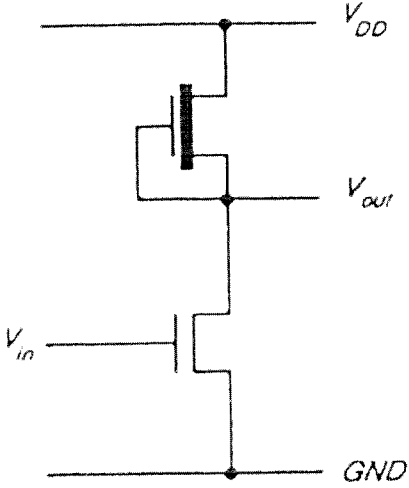
Q No	Solution	Scheme of Marking	Max. Time required for each Question
1	 <p>With no current drawn from the output, the currents <math>I_{ds}</math> for both transistors must be equal.</p> <ul style="list-style-type: none"> <li>• For the depletion mode transistor, the gate is connected to the source so it is always on and only the characteristic curve <math>V_{gs} = 0</math> is relevant.</li> <li>• In this configuration the depletion mode device is called the pull-up (p.u.) and the enhancement mode device the pull-down (p.d.) transistor.</li> <li>• To obtain the inverter transfer characteristic we superimpose the <math>V_{gs} = 0</math> depletion mode characteristic curve on the family of curves for the enhancement mode device, noting that maximum voltage across the enhancement mode device corresponds to minimum voltage across the depletion mode transistor.</li> <li>• The points of intersection of the curves as in Figure <math>f-6</math> give points on the transfer characteristic, which is of the form shown in Figure 2.7.</li> <li>• Note that as <math>V_{in}(=V_{gs}</math> p.d. transistor) exceeds the p.d. threshold voltage current begins to flow. The output voltage <math>V_{out}</math> thus decreases and the subsequent increases in <math>V_{in}</math> will cause the p.d. transistor to come out of saturation and become resistive. Note that the p.u. transistor is initially resistive as the p.d. turns on.</li> </ul>	2+3=5	5
2		5	5

 

3


3+2=5

5

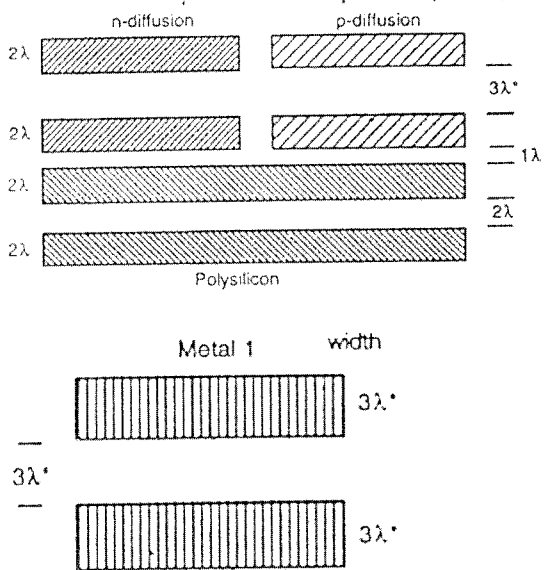



Minimum size transistors

 

Part C

(1Q x 15M = 15Marks)

Q No	Solution	Scheme of Mark	Max. Time require
------	----------	----------------	-------------------

		ing	d for each Question
1	<p style="text-align: center;"><math>I_{ds} = -I_{sd} = \frac{\text{Charge induced in channel } (Q_c)}{\text{Electron transit time } (\tau)}</math></p> <p>First, transit time:</p> $\tau_{sd} = \frac{\text{Length of channel } (L)}{\text{Velocity } (v)}$ <p>but velocity</p> $v = \mu E_{ds}$ <p>where</p> <p style="margin-left: 40px;"><math>\mu</math> = electron or hole mobility (surface)  <math>E_{ds}</math> = electric field (drain to source)</p> <p>Now</p> $E_{ds} = \frac{V_{ds}}{L}$ <p>so that</p> $v = \frac{\mu V_{ds}}{L}$ <p>Thus</p> $\tau_{sd} = \frac{L^2}{\mu V_{ds}}$ <p>Typical values of <math>\mu</math> at room temperature are:</p> <p style="margin-left: 40px;"><math>\mu_n \doteq 650 \text{ cm}^2/\text{V sec}</math> (surface)  <math>\mu_p \doteq 240 \text{ cm}^2/\text{V sec}</math> (surface)</p> <p><b>The Non-saturated Region</b></p>	15	30

Note that the charge/unit area =  $E_g \epsilon_{ins} \epsilon_0$ . Thus induced charge

$$Q_c = E_g \epsilon_{ins} \epsilon_0 WL$$

where

$E_g$  = average electric field gate to channel

$\epsilon_{ins}$  = relative permittivity of insulation between gate and channel

$\epsilon_0$  = permittivity of free space

(Note:  $\epsilon_0 = 8.85 \times 10^{-14} \text{F cm}^{-1}$ ;  $\epsilon_{ins} \approx 4.0$  for silicon dioxide)

Now

$$E_g = \frac{\left( (V_{gs} - V_t) - \frac{V_{ds}}{2} \right)}{D}$$

where  $D$  = oxide thickness.

Thus

$$Q_c = \frac{WL \epsilon_{ins} \epsilon_0}{D} \left( (V_{gs} - V_t) - \frac{V_{ds}}{2} \right) \quad ($$

Now, combining equations (2.2) and (2.3) in equation (2.1), we have

$$I_{ds} = \frac{\epsilon_{ins} \epsilon_0 \mu}{D} \frac{W}{L} \left( (V_{gs} - V_t) - \frac{V_{ds}}{2} \right) V_{ds}$$

The factor  $WL$  is, of course, contributed by the geometry and it is common practice to write

$$\beta = K \frac{W}{L}$$

or

$$I_{ds} = K \frac{W}{L} \left( (V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right)$$

in the non-saturated or resistive region where  $V_{ds} < V_{gs} - V_t$  and

$$K = \frac{\epsilon_{ins} \epsilon_0 \mu}{D}$$

so that

$$I_{ds} = \beta \left( (V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right)$$

which is an alternative form of equation (2.4).

Noting that gate/channel capacitance

$$C_g = \frac{\epsilon_{ins} \epsilon_0 WL}{D} \text{ (parallel plate)}$$

we also have

$$K = \frac{C_g \mu}{WL}$$

so that

$$I_{ds} = \frac{C_g \mu}{L^2} \left( (V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right)$$

## The Saturated Region

*Saturation* begins when  $V_{ds} = V_{gs} - V_t$ , since at this point the  $IR$  drop in the channel equals the effective gate to channel voltage at the drain and we may assume that the current remains fairly constant as  $V_{ds}$  increases further. Thus

$$I_{ds} = K \frac{W}{L} \frac{(V_{gs} - V_t)^2}{2}$$

$$I_{ds} = \frac{\beta}{2} (V_{gs} - V_t)^2$$

$$I_{ds} = \frac{C_g \mu}{2L^2} (V_{gs} - V_t)^2$$

$$I_{ds} = C_0 \mu \frac{W}{L} (V_{gs} - V_t)^2$$

--	--	--	--





Roll No																			
---------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**PRESIDENCY UNIVERSITY  
BENGALURU**

**SCHOOL OF ENGINEERING**

**END TERM FINAL EXAMINATION**

**Semester:** Odd Semester: 2019 - 20

**Date:** 28 December 2019

**Course Code:** ECE 215

**Time:** 9:30 AM to 12:30 PM

**Course Name:** VLSI DESIGN

**Max Marks:** 80

**Program & Sem:** B.Tech (ECE) & VII

**Weightage:** 40%

**Instructions:**

- (i) Read the all questions carefully and answer accordingly.
- (ii) Scientific and Non- programmable calculators are permitted
- (iii) This question paper contains Two pages

**Part A [Memory Recall Questions]**

**Answer all the Questions. Each Question carries 2 marks.**

**(10Qx2M=20M)**

(C.O.No.1-5) [Knowledge]

1. What is Synthesis and Simulation?
2. Define Data Flow style of modeling?
3. Write the equation for Figure of Merit?
4. Define Body effect in NMOS device?
5. Draw the Stick encoding for Polysilicon and write its color?
6. Write the condition for NMOS transistor to be in Non-Saturation region?
7. Name three dynamic logics used to design digital circuits?
8. How many address lines and data lines are required for 8X4 ROM?
9. Write the expression for voltage gain for Common Drain configuration?
10. Draw the basic circuit for Common Source configuration?

**Part B [Thought Provoking Questions]**

**Answer all the Questions. Each Question carries 4 marks.**

**(5Qx6M=30M)**

[Comprehension]

11. Write a Verilog Module and Test Bench for 4X1 MUX in Dataflow style? (C.O.No.1)
12. Draw the Circuit and Stick Diagram for CMOS OAI gate with color representation? (C.O.No.3)
13. Design 8X4 ROM using MOS Transistors with necessary truth table? (C.O.No.4)
14. Design SRAM Memory for storing 8 bits of data in 4 memory locations using SRAM Cells? (C.O.No.4)

15. Design the circuit for the following function in Dynamic CMOS logic?

(C.O.No.4)

$$Z = \overline{A + (B.C)}$$

**Part C [Problem Solving Questions]**

Answer both the Questions. Each Question carries 15 marks.

(2Qx15M=30M)

[Application]


16. A) Explain the operation of CMOS Inverter with neat sketch? (C.O.No.2)

B) For the below circuit find  $I_D$  and  $V_{DS}$ ? In which region the transistor is operating?

Justify

$V_t=1.5V$ ,  $\beta = 1$ ,  $V_g=4V$ ,  $V_{dd}=5V$ ,  $R_D=1 K \text{ ohm}$

(C.O.No.2)

 

17. A) Draw the Basic Current Mirror circuit and write the equation for  $I_{ref}$

(C.O.No.5)

B) An Enhancement PMOS transistor has  $\beta = \frac{80\mu A}{V^2}$ ,  $V_t=-1.5V$ ,  $\lambda = -0.02 V^{-1}$ . The Gate is connected to ground and the source to 5 V. Find the Drain current for  $V_d=0V$  and  $-5V$

(C.O.No.5)





## SCHOOL OF ENGINEERING

### END TERM FINAL EXAMINATION

#### Extract of question distribution [outcome wise & level wise]

Q.NO.	C.O.NO (% age of CO)	Unit/Module Number/Unit  /Module Title	Memory recall type	Thought provoking type	Problem Solving type  [Marks allotted]	Total Marks
			[Marks allotted] Bloom's Levels	[Marks allotted] Bloom's Levels		
			K	C	A	
<b>PART A</b>						
1-2	1	1	4			20
3-4	2	2	4			
5-6	3	3	4			
7-8	4	4	4			
9-10	5	5	4			
<b>PART B</b>						
1	1	1		6		30
2	3	3		6		
3	4	4		6		
4	4	4		6		
5	4	4		6		
<b>PART C</b>						
1	2	2	5		10	30
2	5	5	5		10	
<b>Total Marks</b>			30	30	20	80

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.

I hereby certify that all the questions are set as per the above guidelines.

Faculty Signature:

Reviewer Comment<sup>t</sup>:

Everything o.k. except Part B (Thought Provoking Questions). Faculty member has to comply next sem. onwards.

## Format of Answer Scheme



## SCHOOL OF ENGINEERING

### SOLUTION

Semester: Odd Sem. 2019-20

Course Code: ECE215

Course Name: VLSI Design

Program & Sem: B.Tech & 7<sup>th</sup>

Date: 28.12.2019

Time: 3 HRS


Max Marks: 80

Weightage: 40%

### Part A


(10Q x 2M = 20Marks)

### 5 Minutes for reading Question Paper

Q No	Solution	Scheme of Marking	Max. Time required for each Question (MIN)
1	Generating gate level netlist is called synthesis, Functional verification of a design is called simulation	2	2
2	Dataflow is defined as set of concurrent statements	2	2
3	$\omega_0 = \frac{g_m}{C_g} = \frac{\mu}{L^2} (V_{gs} - V_t) \left( = \frac{1}{\tau_{sd}} \right)$	2	2
4	The <i>body effects</i> may also be taken into account since the substrate may be biased with respect to the source Increasing $V_{SB}$ causes the channel to be depleted of charge carriers and thus the threshold voltage is raised. Change in $V_t$ is given by $\Delta V_t \doteq \gamma(V_{SB})^{1/2}$ where $\gamma$ is a constant which depends on substrate doping so that the more lightly doped the substrate, the smaller will be the body effect.	2	2
5	RED  Polysilicon	2	2
6	$\begin{aligned} V_{gs} &> V_t \\ V_{ds} &< V_{gs} - V_t \end{aligned}$	2	2
7	Dynamic CMOS, Clocked CMOS, CMOS Domino Logic	2	2
8	3,4	2	2
9	$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$	2	2



10

 

2

2

## Part B

(5Q x 6M = 30 Marks)


Q No	Solution	Scheme of Marking	Max. Time required for each Question															
1	<div style="display: flex; justify-content: space-around;"> <table border="1" style="border-collapse: collapse;"> <tr><td>s1</td><td>s0</td><td>z</td></tr> <tr><td>0</td><td>0</td><td>a</td></tr> <tr><td>0</td><td>1</td><td>b</td></tr> <tr><td>1</td><td>0</td><td>c</td></tr> <tr><td>1</td><td>1</td><td>d</td></tr> </table> </div> <pre> Module timescale 1ms/1ns; module mux(z,s,a,b,c,d), output z; input [1:0] s; input a,b,c,d; assign z = (~s1 &amp; s0 &amp; a)              (~s1 &amp; s0 &amp; ~b)              (s1 &amp; ~s0 &amp; c)              (s1 &amp; s0 &amp; ~d); endmodule </pre> <div style="display: flex; justify-content: space-around;"> <pre> Test Bench: timescale 1ms/1ns; module mux_tb(s); wire z; reg a,b,c,d,s; mux m1(z,s,a,b,c,d); initial begin s=0; a=0; b=1; c=0; d=1; #2 s=1'b01; #10 \$stop; end endmodule </pre> </div>	s1	s0	z	0	0	a	0	1	b	1	0	c	1	1	d	1/2+1/2+3+2	20
s1	s0	z																
0	0	a																
0	1	b																
1	0	c																
1	1	d																

<p>2</p>	<p><u>OAI gate:</u>  <math>Z = (A+B)(C+D)</math></p>	<p>3+3</p>	<p>20</p>
<p>3</p>		<p>2+3+1</p>	<p>15</p>
<p>4</p>	<p><u>SRAM:</u> 4 memory locations 8 bits</p>	<p>2+3+1</p>	<p>15</p>



5

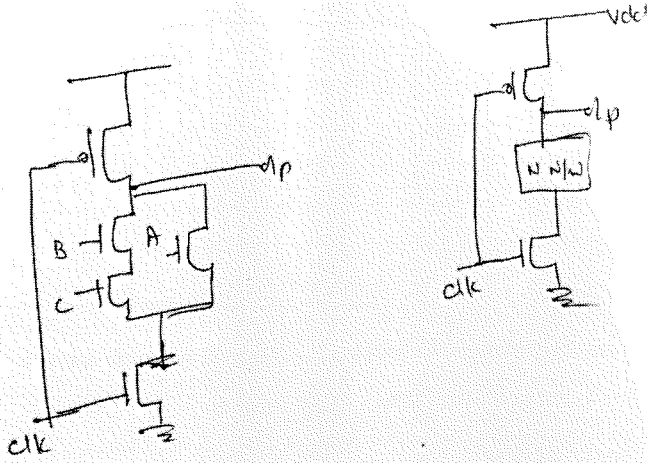$z = \overline{A+(B \cdot C)}$  in dynamic CMOS logic





1+1+4

15



Part C

(2Q x 15M = 30Marks)


Q No	Solution	Scheme of Marking	Max. Time required for each Question
1	<p>(a) No current flow either for logical 0 or for logical 1 inputs.                      (b) Full logical 1 and 0 levels are presented at the output.                      (c) For devices of similar dimensions the p-channel is slower than the n-channel device.</p> <div style="display: flex; justify-content: space-around;"> <div data-bbox="242 1115 427 1496"> <p>(a) Circuit</p> </div> <div data-bbox="545 1070 954 1518"> <p>(b) Transfer characteristic</p> </div> </div>	<p>2+4+3+3+3</p> 	<p>35</p> 

For the circuit shown, use the the NMOS equations to find  $i_D$  and  $v_{DS}$ .

For the NMOS,  $V_T = 1.5 \text{ V}$  and  $K = 0.5 \text{ mA/V}^2$ .

$v_{GS} = V_G = 4 \text{ V} \rightarrow$  the NMOS is on.

 Assume that the transistor is in saturation.





$$i_D = K(v_{GS} - V_T)^2 = (0.5 \text{ mA/V}^2) [4 \text{ V} - 1.5 \text{ V}]^2 = 3.125 \text{ mA}$$

$$v_{DS} = V_{DD} - i_D R_D = 10 \text{ V} - (3.125 \text{ mA})(2 \text{ k}\Omega) = 3.75 \text{ V}$$

$$v_{GS} - V_T = 4 \text{ V} - 1.5 \text{ V} = 2.5 \text{ V}$$

$v_{DS} > v_{GS} - V_T \rightarrow$  saturation confirmed.

2

  

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2$$

Case 3:  $V_D = 0 \text{ V}$ ,

$V_{SD} = 5 - 0 = 5 \text{ V} > |V_i| \Rightarrow$  not cutoff!  $V_{DG} = 0 - 0 = 0 \text{ V} \leq |V_i| \Rightarrow$  in Saturation!

$$I_D = \frac{k'_p}{2} \times \frac{W}{L} (V_{SD} - |V_i|)^2 (1 + |\lambda| V_{SD})$$

$$I_D = \frac{80 \times 10^{-6}}{2} (5 - |-1.5|)^2 [1 + |-0.02| \times (5 - 0)] \rightarrow I_D = 40 \times 10^{-6} \times 3.5^2 \times 1.1 = 539 \mu\text{A}$$

3+4+4+4

35

