



# PRESIDENCY UNIVERSITY

BENGALURU

Roll No.												
----------	--	--	--	--	--	--	--	--	--	--	--	--

## End - Term Examinations – MAY 2025

Date: 29-05-2025

Time: 01:00 pm – 04:00 pm

<b>School:</b> SOE/SOCSE	<b>Program:</b> B.Tech – Basic Engineering Science Cycle	
<b>Course Code:</b> EEE1007	<b>Course Name:</b> Basics of Electrical and Electronics Engineering	
<b>Semester:</b> II	<b>Max Marks:</b> 100	<b>Weightage:</b> 50%

CO - Levels	CO1	CO2	CO3	CO4	CO5
Marks	24	24	26	26	

### Instructions:

- (i) Read all questions carefully and answer accordingly.
- (ii) Do not write anything on the question paper other than roll number.

### Part A

Answer ALL the Questions. Each question carries 2marks.

10Q x 2M=20M

1.	What is the equivalent resistance, if there are three resistors connected in series.	2 Marks	L1	CO1
2.	Write the relationship between line voltage and phase voltage in a three-phase, star-connected network.	2 Marks	L1	CO1
3.	List any two differences between a conductor, insulator and semiconductor.	2 Marks	L1	CO2
4.	Why is a capacitive filter included at the output of a rectifier.	2 Marks	L1	CO2
5.	What is the basic principle behind the working of a transformer.	2 Marks	L1	CO3
6.	Write the expression to calculate the Back EMF of a DC motor.	2 Marks	L1	CO3
7.	What are the two types of rotors used in an induction motor.	2 Marks	L1	CO3
8.	Define a transistor.	2 Marks	L1	CO4
9.	For a BJT to operate in active region, what should be the biasing condition of the emitter-base junction and collector-base junction.	2 Marks	L1	CO4


10.	Name all the three terminals of an E-MOSFET.	2 Marks	L1	C04
-----	--	---------	----	-----

## Part B

### Answer the Questions.

Total Marks 80M

11.	a.	With examples, explain the classification of elements based on (i) Ability to deliver power, (ii) Size of the element	10 Marks	L2	C01
	b.	A series R-L-C network consists of $25\Omega$ resistor, $12\Omega$ inductive reactance and $38\Omega$ capacitive reactance. A voltage source ( $V_{rms}$ ) of 230V is supplied and a current ( $I_{rms}$ ) of 6.4A is observed. Calculate (i) impedance, (ii) phase, (iii) power and (iv) power factor of the network.	10 Marks	L2	C01
Or					
12.	a.	Draw the circuit diagram and phasor diagram for a series resistive-inductive-capacitive (RLC) network. Explain the phasor diagram.	10 Marks	L2	C01
	b.	A $20\Omega$ resistor is connected in series, with a parallel combination of $50\Omega$ and $100\Omega$ resistors. If the voltage supplied to the resistors is 50V, calculate the power consumed by the all the three resistors.	10 Marks	L2	C01

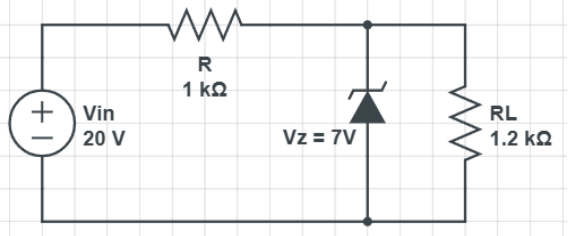13.	a.	Sketch the I-V characteristics of a p-n junction diode in both forward-bias and reverse-bias condition. Label and explain (i) Knee voltage, (ii) Static resistance, (iii) Dynamic resistance	10 Marks	L2	C02
	b.	Explain the (i) ideal diode model and (ii) piece-wise linear diode model with appropriate diagrams.	10 Marks	L2	C02
Or					
14.	a.	With the help of a circuit diagram and appropriate waveforms, explain the working of a half-wave rectifier without and with a capacitive filter.	10 Marks	L2	C02
	b.	For the circuit shown below, determine (i) load voltage ( $V_L$ ), (ii) resistive voltage ( $V_R$ ) and (iii) Zener current ( $I_Z$ ). 	10 Marks	L2	C02

15.	a.	With the help of appropriate diagrams, describe the construction of a single-phase transformer, and explain its working.	10 Marks	L2	C03
-----	----	--	----------	----	-----

	<b>b.</b>	Explain the different types of DC machines. Compare the speed-torque characteristics of each motor type.	10 Marks	<b>L2</b>	<b>CO3</b>
<b>Or</b>					
<b>16.</b>	<b>a.</b>	With neat diagram, explain the construction of a three-phase induction motor.	10 Marks	<b>L2</b>	<b>CO3</b>
	<b>b.</b>	Describe the construction of a permanent magnet DC motor, and explain its working principle.	10 Marks	<b>L2</b>	<b>CO3</b>

<b>17.</b>	<b>a.</b>	Draw the input characteristics and output characteristics of a common-base configured npn transistor. Explain the relationship between the current and voltage in each case.	10 Marks	<b>L2</b>	<b>CO4</b>
	<b>b.</b>	For a npn transistor, derive the relationship between (i) Common-base gain ( $\alpha$ ) and Common-emitter gain ( $\beta$ ) (ii) Common-emitter gain ( $\beta$ ) and Common-collector gain ( $\gamma$ )	10 Marks	<b>L2</b>	<b>CO4</b>
<b>Or</b>					
<b>18.</b>	<b>a.</b>	Draw the transfer characteristics and output characteristics of a n-channel JFET. Label and explain ohmic region, saturation region and breakdown region.	10 Marks	<b>L2</b>	<b>CO4</b>
	<b>b.</b>	With a neat sketch of a n-channel enhancement type MOSFET, explain the working of the E-MOSFET under the following conditions. (i) $V_{GS} = 0V$ , $V_{DS} = \text{positive}$ ,    (ii) $V_{GS} = \text{positive}$ , $V_{DS} = \text{positive}$ .	10 Marks	<b>L2</b>	<b>CO4</b>