



Roll No.											
----------	--	--	--	--	--	--	--	--	--	--	--

PRESIDENCY UNIVERSITY

BENGALURU

Mid - Term Examinations – October 2025

Date: 09-10-2025

Time: 02.00pm to 03.30pm

School: SOIS	Program: BCA, BCA(DS), BCA(AIML)	
Course Code : CSA1200	Course Name: Digital Computer Fundamentals	
Semester: I	Max Marks: 50	Weightage: 25%

CO – Levels	CO1	CO2	CO3	CO4	CO5
Marks	36	14	-	-	-

Instructions:

- (i) *Read all questions carefully and answer accordingly.*
- (ii) *Do not write anything on the question paper other than roll number.*

Part A

Answer ALL the Questions. Each question carries 2marks.

5Q x 2M=10M

1	State absorption law.	2 Marks	L1	CO1
2	What is Boolean algebra?	2 Marks	L1	CO1
3	Show that $(A'(A'+1))' = A$	2 Marks	L1	CO1
4	Compare multiplexer and demultiplexer.	2 Marks	L1	CO2
5	Define combinational circuits.	2 Marks	L1	CO2

Part B

Answer the Questions.

Total Marks 40M

6.	a.	Determine sum of product terms from the given Boolean expression $F(A, B, C, D) = (A'+B+D). (A+C'+D). (A'+B'+C'). (A+B+C)$.	15 Marks	L3	CO 1
	b.	Implement XOR and XNOR using NAND gates	5 Marks	L2	CO 1

Or

7.	a.	Compute simplified product of sum from the Boolean expression $F(A, B, C, D) = AC+B'D$	15 Marks	L3	CO 1
	b.	Discuss in detail about 3 variable k-map.	5 Marks	L2	CO 1

8.	a.	State and prove De morgan's law.	10 Marks	L	CO 1
	b.	Describe about Full adder. How full adder can be constructed using half adders?	10 Marks	L	CO 2
Or					
9.	a.	Compute equivalent value of hexadecimal, decimal and binary for the octal number $(456)_8$.	10 Marks	L	CO 1
	b.	Describe about Full subtractor. How full subtractor can be constructed using half subtractors?	10 Marks	L	CO 2