

3. What are Universal gates? Realize fundamental gates using universal gates

(C.O.NO.1)[Knowledge]

4. Write the Truth Table and Logic circuit using basic gates for the following expression

a. $F1 = x + y'z$

b. $F2 = x'z + xy'$

(C.O.NO.1)[Knowledge]

Part C [Problem Solving Questions]

Answer the Question. The Question carries seven marks.

(1Qx7M=7M)

5. Simplify $F(A,B,C,D) = \Sigma m(0,1,2,4,5,6,8,9,10,12,13)$

using K-Map and realize the resultant expression using NAND gates only.

(C.O.NO.2)[Comprehension]



SCHOOL OF INFORMATION SCIENCE

Semester. 1

Course Code: BCA 102

Course Name: Digital Electronics

Program & Sem: BCA

Date: 30/09/2019

Time: 9:30am to 10:30am

Max Marks: 40

Weightage: 20%

Extract of question distribution [outcome wise & level wise]

Q.NO	C.O.NO	Unit/Module Number/Unit /Module Title	Memory recall type [Marks allotted] Bloom's Levels			Thought provoking type [Marks allotted] Bloom's Levels			Problem Solving type [Marks allotted]			Total Marks
			K			C			A			
1	CO1	Module1		12								12
2	CO1	Module1		18								18
3	CO2	Module2					10					10
	Total Marks			30			10					40

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.

[I hereby certify that All the questions are set as per the above guide lines. Srivinay]

Reviewers' Comments



SCHOOL OF INFORMATION SCIENCE

SOLUTION

Semester: 1

Course Code: BCA 102

Course Name: Digital Electronics

Program & Sem: BCA

Date: 30/09/2019

Time: 9:30am to 10:30am

Max Marks: 40

Weightage: 20%

Part A

(1Q x 12 M = 12 Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question
1	a. $(3039)_{16}$ $(30071)_8$ b. $(DBF5)$ c. $(12345)_{10}$ d. $(23567)_{10}$	3M each	15 min

Part B

(3Q x 6M = 18 Marks)


Q No	Solution	Scheme of Marking	Max. Time required for each Question
------	----------	-------------------	--------------------------------------

x	y	$x + y$	$(x + y)'$	x'	y'	$x'y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

DATE: / /
Proof- 5M

5 min

3.

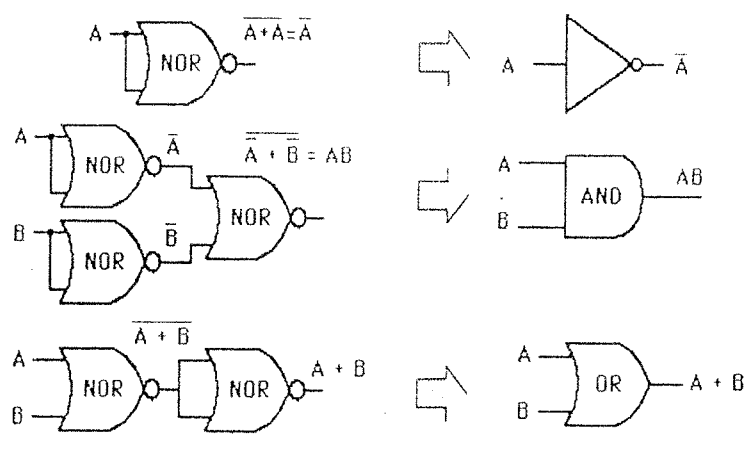

Defn: 1M
NOR: 1M
AND: 2M
OR: 2M

10 min



4.

T.T = 3M
Circuit = 3M

15 min

Truth Table for F_1 and F_2

x	y	z	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

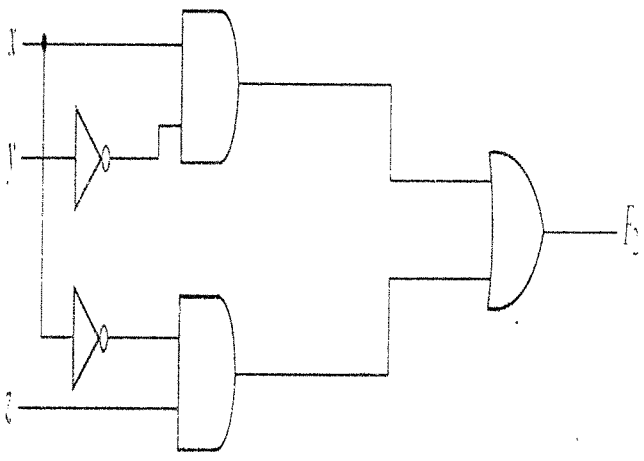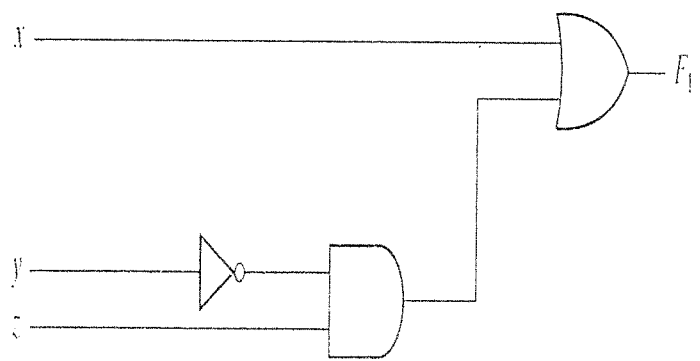

(b) $F_2 = xy' + x'z$

Part C

(1Q x10 M =10 Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question																																																								
5.	<table border="1" style="margin-bottom: 10px;"> <thead> <tr> <th></th> <th>$\bar{C}\bar{D}$</th> <th>$\bar{C}D$</th> <th>CD</th> <th>$C\bar{D}$</th> </tr> </thead> <tbody> <tr> <th>$\bar{A}\bar{B}$</th> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <th>$\bar{A}B$</th> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <th>AB</th> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <th>$A\bar{B}$</th> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table> <p style="text-align: center;">Map Layout</p> <table border="1" style="margin-bottom: 10px;"> <thead> <tr> <th></th> <th>$\bar{C}\bar{D}$</th> <th>$\bar{C}D$</th> <th>CD</th> <th>$C\bar{D}$</th> </tr> </thead> <tbody> <tr> <th>$\bar{A}\bar{B}$</th> <td>0</td> <td>1</td> <td>3</td> <td>2</td> </tr> <tr> <th>$\bar{A}B$</th> <td>4</td> <td>5</td> <td>7</td> <td>6</td> </tr> <tr> <th>AB</th> <td>12</td> <td>13</td> <td>15</td> <td>14</td> </tr> <tr> <th>$A\bar{B}$</th> <td>8</td> <td>9</td> <td>11</td> <td>10</td> </tr> </tbody> </table> <p style="text-align: center;">Groups</p> <table border="1" style="margin-bottom: 10px;"> <tbody> <tr> <td>(0,1,4,5,8,9,12,13)</td> <td>\bar{C}</td> </tr> <tr> <td>(0,2,4,6)</td> <td>$\bar{A}\bar{D}$</td> </tr> <tr> <td>(0,2,8,10)</td> <td>$\bar{B}\bar{D}$</td> </tr> </tbody> </table> <p>$y = \bar{C} - \bar{A}\bar{D}' - \bar{B}\bar{D}$</p>		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	$\bar{A}\bar{B}$	1	1	0	1	$\bar{A}B$	1	1	0	1	AB	1	1	0	0	$A\bar{B}$	1	1	0	1		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	$\bar{A}\bar{B}$	0	1	3	2	$\bar{A}B$	4	5	7	6	AB	12	13	15	14	$A\bar{B}$	8	9	11	10	(0,1,4,5,8,9,12,13)	\bar{C}	(0,2,4,6)	$\bar{A}\bar{D}$	(0,2,8,10)	$\bar{B}\bar{D}$	<p>Writing K-map – 2M</p> <p>Grouping – 6M</p> <p>Nand Implementation – 2M</p>	15min
	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$																																																							
$\bar{A}\bar{B}$	1	1	0	1																																																							
$\bar{A}B$	1	1	0	1																																																							
AB	1	1	0	0																																																							
$A\bar{B}$	1	1	0	1																																																							
	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$																																																							
$\bar{A}\bar{B}$	0	1	3	2																																																							
$\bar{A}B$	4	5	7	6																																																							
AB	12	13	15	14																																																							
$A\bar{B}$	8	9	11	10																																																							
(0,1,4,5,8,9,12,13)	\bar{C}																																																										
(0,2,4,6)	$\bar{A}\bar{D}$																																																										
(0,2,8,10)	$\bar{B}\bar{D}$																																																										



Roll No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**PRESIDENCY UNIVERSITY
BENGALURU**

SCHOOL OF INFORMATION SCIENCE

TEST – 2

Sem & AY: Odd Sem 2019-20

Date: 18.11.2019

Course Code: BCA102

Time: 9:30 AM to 10:30 AM

Course Name: DIGITAL ELECTRONICS

Max Marks: 30

Program & Sem: BCA & I

Weightage: 15%

Instructions:

- (i) Read the question properly and answer accordingly.
- (ii) Question paper consists of 3 parts.
- (iii) Scientific and Non-programmable calculators are permitted.

Part A [Memory Recall Questions]

1. Answer all the Questions. Each Question carries one mark. (4Qx1M=4M)

- i. There are _____ cells in a 4-variable K-map.
a. 12 b. 16 c. 18 d. 8
- ii. What is the function of an enable input on a multiplexer chip?
a. To apply V_{cc}
b. To connect ground
c. To active the entire chip
d. To active one half of the chip
- iii. How many select lines would be required for a 32-line-to-1-line multiplexer?
a. 2 b. 4 c. 8 d. 5
- iv. The prime implicant which has at least one element that is not present in any other implicant is known as _____
a. Essential Prime Implicant
b. Implicant
c. Complement
d. Prime Complement

(C.O.NO.1) [Knowledge]

Part B [Thought Provoking Questions]

Answer both the Questions. Each Question carries six marks. (2Qx6M=12M)

(C.O.NO.3) [Application]

2. Show how 8:1 Multiplexer can be obtained by using only 2:1 Multiplexer.
3. With a neat block diagram, truth table and logic circuit. Explain the working of a Half Adder and Full Adder.

Part C [Problem Solving Questions]

Answer both the Questions.

(2Q=14M)

(C.O.NO.2) [Application]

4. Simplify $F(A,B,C,D) = \sum m(0,1,2,3,10,11,12,13,14,15)$ using QM method. Implement the resultant expression using NAND gates only. [10 M]
5. Simplify $F(A,B,C,D) = \sum m(0,2,4,6,8,9,10,12,14) + d(1,5,11,13)$ using K-map [4 M]



SCHOOL OF INFORMATION SCIENCE

Semester: 1
 Course Code: BCA 102
 Course Name: Digital Electronics
 Program & Sem: BCA

Date: 18/11/2019
 Time: 9:30am to 10:30am
 Max Marks: 30
 Weightage: 15%

Extract of question distribution [outcome wise & level wise]

Q.NO	C.O.NO	Unit/Module Number/Unit /Module Title	Memory recall type		Thought provoking type			Problem Solving type		Total Marks
			[Marks allotted]	Bloom's Levels	[Marks allotted]	Bloom's Levels	[Marks allotted]	Bloom's Levels		
				K		C		A		
1	CO1	Module2,3		4					4	
2	CO3	Module3					12		12	
3	CO2	Module2					14		14	
	Total Marks			4		00		26	30	

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.



SCHOOL OF INFORMATION SCIENCE

SOLUTION

Semester: 1

Course Code: BCA 102

Course Name: Digital Electronics

Program & Sem: BCA

Date: 30/09/2019

Time: 9:30am to 10:30am

Max Marks: 40

Weightage: 20%

Part A

(4Q x 1 M = 4 Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question
1	i. 16 ii. To active the entire chip iii. 5 iv. Essential Prime Implicant	1M each	5 min

Part B

(2Q x 6M = 12 Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question																				
2.	<p style="text-align: center;">4 x 5 Multiplexer</p>	Expression: 2M Diagram- 4M	10 min																				
3.	<p>Table 4-3 Half Adder</p> <table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>C</th> <th>S</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	x	y	C	S	0	0	0	0	0	1	0	1	1	0	0	1	1	1	1	0	Half Adder 3M Full Adder 3M	10 min
x	y	C	S																				
0	0	0	0																				
0	1	0	1																				
1	0	0	1																				
1	1	1	0																				

--	--	--	--

Part C

Q No	Solution	Scheme of Marking	Max. Time required for each Question																																																						
4.	Prime Implicants $A'B', B'C, AC, AB$ EPI $Y = A'B' + AC + AB$	PI Table : 4M EPI Table: 3M NAND circuit: 4M	25 min																																																						
5.	<p align="center">Map</p> <table border="1"> <tr> <td></td> <td>C.D</td> <td>C.D</td> <td>C.D</td> <td>C.D</td> </tr> <tr> <td>A.B</td> <td>1</td> <td>x</td> <td>0</td> <td>1</td> </tr> <tr> <td>A.B</td> <td>1</td> <td>x</td> <td>0</td> <td>1</td> </tr> <tr> <td>A.B</td> <td>1</td> <td>x</td> <td>0</td> <td>1</td> </tr> <tr> <td>A.B</td> <td>1</td> <td>1</td> <td>x</td> <td>1</td> </tr> </table> <p align="center">Map Layout</p> <table border="1"> <tr> <td></td> <td>C.D</td> <td>C.D</td> <td>C.D</td> <td>C.D</td> </tr> <tr> <td>A.B</td> <td>0</td> <td>1</td> <td>3</td> <td>2</td> </tr> <tr> <td>A.B</td> <td>4</td> <td>5</td> <td>7</td> <td>6</td> </tr> <tr> <td>A.B</td> <td>12</td> <td>13</td> <td>15</td> <td>14</td> </tr> <tr> <td>A.B</td> <td>8</td> <td>9</td> <td>11</td> <td>10</td> </tr> </table> <p align="center">Groups</p> <table border="1"> <tr> <td>(0,2,4,6,8,10,12,14)</td> <td>D</td> </tr> <tr> <td>(0,1,4,5,8,9,12,13)</td> <td>C</td> </tr> </table> $y = D' + C'$		C.D	C.D	C.D	C.D	A.B	1	x	0	1	A.B	1	x	0	1	A.B	1	x	0	1	A.B	1	1	x	1		C.D	C.D	C.D	C.D	A.B	0	1	3	2	A.B	4	5	7	6	A.B	12	13	15	14	A.B	8	9	11	10	(0,2,4,6,8,10,12,14)	D	(0,1,4,5,8,9,12,13)	C	Grouping: 2M Writing Expression: 2M	10 min
	C.D	C.D	C.D	C.D																																																					
A.B	1	x	0	1																																																					
A.B	1	x	0	1																																																					
A.B	1	x	0	1																																																					
A.B	1	1	x	1																																																					
	C.D	C.D	C.D	C.D																																																					
A.B	0	1	3	2																																																					
A.B	4	5	7	6																																																					
A.B	12	13	15	14																																																					
A.B	8	9	11	10																																																					
(0,2,4,6,8,10,12,14)	D																																																								
(0,1,4,5,8,9,12,13)	C																																																								



Roll No																			
---------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**PRESIDENCY UNIVERSITY
BENGALURU**

SCHOOL OF INFORMATION SCIENCE

END TERM FINAL EXAMINATION

Semester: Odd Semester: 2019-20

Date: 03 January 2020

Course Code: BCA 102

Time: 1:00 PM to 4:00 PM

Course Name: DIGITAL ELECTRONICS

Max Marks: 100

Program & Sem: BCA & I

Weightage: 50%

Instructions:

(i) Read all questions carefully and answer accordingly.

Part A [Memory Recall Questions]

Answer all the Questions. Each Question carries 8 marks.

(2Qx8M=16M)

1. Convert the following:

(C.O.No.1) [Knowledge]

i. $(12345)_{10} = (?)_{16} = (?)_8$

ii. $(1101101111110101)_2 = (?)_{16}$

iii. $(11000000111001)_2 = (?)_{10}$

iv. $(56017)_8 = (?)_{10}$

2. a) State and Prove De-Morgan's theorem.

(C.O.No.1) [Knowledge]

b) Realize Basic gates using Universal gates.

Part B [Thought Provoking Questions]

Answer all the Questions. Each Question carries 10 marks.

(6Qx10M=60M)

3. With a neat block diagram, truth table and logic circuit. Explain the working of a Half Adder and Full Adder.

(C.O.No.3) [Comprehension]

4. Show how 8:1 Multiplexer can be obtained by using only 2:1 Multiplexer along with the boolean expression

(C.O.No.3) [Application]

5. With a neat logic diagram, explain the working of a BCD to Excess3 code converter.

(C.O.No.3) [Comprehension]

6. What is the difference between a Latch and a Flip-flop? Show the state transition diagram of SR, D, JK, and T Flip-flops.

(C.O.No.3) [Application]

7. With a neat logic circuit, logic symbol, and characteristic table, explain the working of negative edge triggered JK-Flip-flop. (C.O.No.3) [Comprehension]

8. With a neat logic diagram, explain the working of a 3-bit Ripple counter. (C.O.No.3) [Comprehension]

Part C [Problem Solving Questions]

Answer both the Questions. Each Question carries 12 marks. (2Qx12M=24M)

9. a) Simplify $F(A,B,C,D) = \sum m(0,1,2,4,5,6,8,9,10,12,13)$ using K-Map and realize the resultant expression using NAND gates only. (C.O.No.2) [Application]

b) Simplify $F(A,B,C,D) = \sum m(0,2,4,6,8,9,10,12,14) + d(1,5,11,13)$ using K-map

10. Simplify $F(A,B,C,D) = \sum m(0,1,2,3,10,11,12,13,14,15)$ using QM method. Implement the resultant expression using NAND gates only. (C.O.No.2) [Application]



SCHOOL OF INFORMATION SCIENCE

END TERM FINAL EXAMINATION

Extract of question distribution [outcome wise & level wise]

Q.NO.	C.O. NO (% age of CO)	Unit/Module Number/Unit /Module Title	Memory recall type	Thought provoking type	Problem Solving type [Marks allotted]	Total Marks
			[Marks allotted]	[Marks allotted]		
			Bloom's Levels	Bloom's Levels		
			K	C	A	
Part A Q. No1	C.O. No.1	Module1	8			8
Part A Q. No2	C.O. No.1	Module1	8			8
Part B Q. No3	C.O. No.3	Module 3		10		10
Part B Q. No4	C.O. No.3	Module 3			10	10
Part B Q. No5	C.O. No.3	Module 3		10		10
Part B Q. No6	C.O. No.3	Module 3			10	10
Part B Q. No7	C.O. No.3	Module 3		10		10
Part B Q. No8	C.O. No.3	Module 3		10		10
Part C Q. No9	C.O. No.2	Module 2			12	10


Part C Q. No10	C.O. No.2	Module 2			12	10
Total Marks			16	40	44	100

K = Knowledge Level C = Comprehension Level, A = Application Level

Note: While setting all types of questions the general guideline is that about 60%

Of the questions must be such that even a below average students must be able to attempt, About 20% of the questions must be such that only above average students must be able to attempt and finally 20% of the questions must be such that only the bright students must be able to attempt.

I hereby certify that all the questions are set as per the above guidelines.

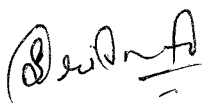Faculty Signature: 

Reviewer Comment:

!b Marks only given for knowledge level.
Discussed with Op setter. Informed me that
students are well trained to solve the part-C,
prob-solving. questions.

R. Peahla
27/12/19.

Format of Answer Scheme



SCHOOL OF ENGINEERING

SOLUTION

Semester: Odd sem 2019-20

Course Code: BCA 102

Course Name: Digital Electronics

Program & Sem: BCA 1st sem

Date: 03 Jan 2020

Time: 1:00pm to 4:00pm

Max Marks: 100

Weightage: 50%

Part A

(2Q x 10M = 20Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question																																			
1	a. $(3039)_{16}$ $(30071)_8$ b. $(DBF5)$ c. $(12345)_{10}$ d. $(23567)_{10}$	2M EACH	10min																																			
2.a)	<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>x</th> <th>y</th> <th>$x + y$</th> <th>$(x + y)'$</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table> <table border="1" style="display: inline-table;"> <thead> <tr> <th>x'</th> <th>y'</th> <th>$x'y'$</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	x	y	$x + y$	$(x + y)'$	0	0	0	1	0	1	1	0	1	0	1	0	1	1	1	0	x'	y'	$x'y'$	1	1	1	1	0	0	0	1	0	0	0	0	4M	20min
x	y	$x + y$	$(x + y)'$																																			
0	0	0	1																																			
0	1	1	0																																			
1	0	1	0																																			
1	1	1	0																																			
x'	y'	$x'y'$																																				
1	1	1																																				
1	0	0																																				
0	1	0																																				
0	0	0																																				
2.b)		4M																																				

Part B

(6Q x 10M = 60 Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question																				
3	<p> $C = xy$ $S = x \oplus y$ </p> <p> $C = xy + xz + yz$ </p> <p>Table 4-3 <i>Half Adder</i></p> <table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>C</th> <th>S</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	x	y	C	S	0	0	0	0	0	1	0	1	1	0	0	1	1	1	1	0	<p>Half adder – 5M</p> <p>Full Adder – 5M</p>	<p>20min</p>
x	y	C	S																				
0	0	0	0																				
0	1	0	1																				
1	0	0	1																				
1	1	1	0																				
4		<p>Boolean expression – 4M</p> <p>Circuit—6M</p>	<p>10min</p>																				
5	<p> Excess-3 code can be derived from BCD code by adding 3 to each number. For example, Decimal number 12 is represented as 0001 0010 in BCD. If we add 3 that is to add 0011 0011 then the corresponding Excess-3 code is 0100 0101. </p>	<p>Truth Table –4M</p> <p>K-map – 3M</p> <p>Circuit – 3M</p>	<p>25min</p>																				

6

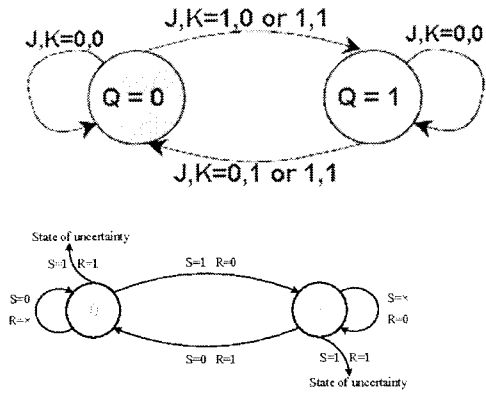


Fig. 5. The state diagram of SR flip-flop circuit ($CP = 1$).

* Latch and Flip-flop are used to store 1 bit. But flipflop is controlled by a clock
 * Latch is a transparent circuit.


Difference- 2M

Each flip-flop transition—2M

20min

7

Inputs			Outputs		Comments
J	K	CLK	Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\bar{Q}_0	Q_0	Toggle

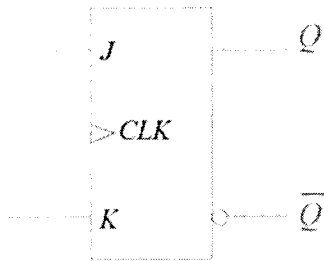

Explanation of truth table is required

Logic circuit – 2M


Logic symbol – 2M

Characteristic table – 3M

Explanation –3M

15min

8

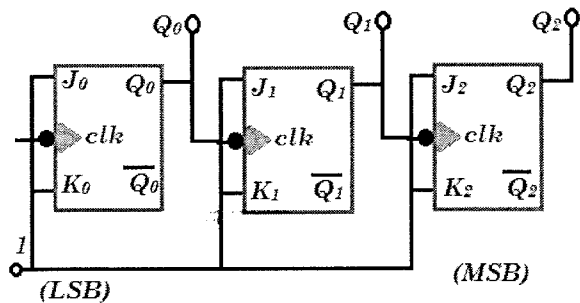

©Elpocus.com

Write the 3 bit truth table and explanation of circuit

Circuit—5M

Table –2M

Explanation – 3M

15min

Part C

(2Q x 12M = 24Marks)

Q No	Solution	Scheme of Marking	Max. Time required for each Question																																																												
9.a)	<p> $\begin{array}{ccccc} & \overline{C}D & \overline{C}D & C.D & C.D \\ \overline{A}B & 1 & 1 & 0 & 1 \\ \overline{A}B & 1 & 1 & 0 & 1 \\ AB & 1 & 1 & 0 & 0 \\ AB & 1 & 1 & 0 & 1 \end{array}$ </p> <p>Map Layout</p> <p> $\begin{array}{ccccc} & \overline{C}D & \overline{C}D & C.D & C.D \\ \overline{A}B & 0 & 1 & 3 & 2 \\ \overline{A}B & 4 & 5 & 7 & 6 \\ AB & 12 & 13 & 15 & 14 \\ AB & 8 & 9 & 11 & 10 \end{array}$ </p> <p>Groups</p> <table border="1" style="margin-left: 20px;"> <tr><td>(0,1,4,5,8,9,12,13)</td><td>\overline{C}</td></tr> <tr><td>(0,2,4,6)</td><td>$\overline{A}D$</td></tr> <tr><td>(0,2,8,10)</td><td>$\overline{B}D$</td></tr> </table> <p>$y = \overline{C} + \overline{A}D + \overline{B}D$</p> <p>Map</p> <table border="1" style="margin-left: 20px;"> <tr><td></td><td>C.D</td><td>C.D</td><td>C.D</td><td>C.D</td></tr> <tr><td>A.B</td><td>1</td><td>x</td><td>0</td><td>1</td></tr> <tr><td>A.B</td><td>1</td><td>x</td><td>0</td><td>1</td></tr> <tr><td>A.B</td><td>1</td><td>x</td><td>0</td><td>1</td></tr> <tr><td>A.B</td><td>1</td><td>1</td><td>x</td><td>1</td></tr> </table> <p>Map Layout</p> <table border="1" style="margin-left: 20px;"> <tr><td></td><td>C.D</td><td>C.D</td><td>C.D</td><td>C.D</td></tr> <tr><td>A.B</td><td>0</td><td>1</td><td>3</td><td>2</td></tr> <tr><td>A.B</td><td>4</td><td>5</td><td>7</td><td>6</td></tr> <tr><td>A.B</td><td>12</td><td>13</td><td>15</td><td>14</td></tr> <tr><td>A.B</td><td>8</td><td>9</td><td>11</td><td>10</td></tr> </table> <p>Groups</p> <table border="1" style="margin-left: 20px;"> <tr><td>(0,2,4,6,8,10,12,14)</td><td>D</td></tr> <tr><td>(0,1,4,5,8,9,12,13)</td><td>C</td></tr> </table>	(0,1,4,5,8,9,12,13)	\overline{C}	(0,2,4,6)	$\overline{A}D$	(0,2,8,10)	$\overline{B}D$		C.D	C.D	C.D	C.D	A.B	1	x	0	1	A.B	1	x	0	1	A.B	1	x	0	1	A.B	1	1	x	1		C.D	C.D	C.D	C.D	A.B	0	1	3	2	A.B	4	5	7	6	A.B	12	13	15	14	A.B	8	9	11	10	(0,2,4,6,8,10,12,14)	D	(0,1,4,5,8,9,12,13)	C	<p>Writing K-map – 2M Grouping – 2M Nand Implementation – 2M</p> <p>Writing K-map – 2M Grouping – 4M</p>	<p>20min</p>
(0,1,4,5,8,9,12,13)	\overline{C}																																																														
(0,2,4,6)	$\overline{A}D$																																																														
(0,2,8,10)	$\overline{B}D$																																																														
	C.D	C.D	C.D	C.D																																																											
A.B	1	x	0	1																																																											
A.B	1	x	0	1																																																											
A.B	1	x	0	1																																																											
A.B	1	1	x	1																																																											
	C.D	C.D	C.D	C.D																																																											
A.B	0	1	3	2																																																											
A.B	4	5	7	6																																																											
A.B	12	13	15	14																																																											
A.B	8	9	11	10																																																											
(0,2,4,6,8,10,12,14)	D																																																														
(0,1,4,5,8,9,12,13)	C																																																														
10	<p>Prime Implicants $A'B', B'C, AC, AB$</p> <p>EPI $Y = A'B' + AC + AB$</p>	<p>PI Table : 5M EPI Table: 4M NAND circuit: 3M</p>	<p>25min</p>																																																												