

Roll No.									
----------	--	--	--	--	--	--	--	--	--



PRESIDENCY UNIVERSITY

BENGALURU

Mid - Term Examinations - October 2025

Date: 09-10-2025

Time: 09.30am to 11.00am

School: SOE	Program: B.Tech		
Course Code : EEE2032	Course Name: Electrical & Electronic Measurements and Instrumentation		
Semester: V	Max Marks: 50	Weightage: 25%	

Instructions:

(i)

CO - Levels	CO1	CO2	CO3	CO4
Marks	18	32	0	0

Read all

questions carefully and answer accordingly.

(ii) Do not write anything on the question paper other than roll number.

Part A

Answer ALL the Questions. Each question carries 2marks.				2Mx5Q=10M
1	What are the primary functional elements of a measurement instrument?	2 Marks	L1	CO1
2	Why is calibration important in measurement systems?	2 Marks	L1	CO1
3	What is the purpose of statistical evaluation in measurement data?	2 Marks	L1	CO1
4	Define the concept of hysteresis in meters.	2 Marks	L1	CO2
5	Recall the concept of True value and Measured value.	2 Marks	L1	CO1

Part B

Answer ALL Questions. Each question carries 10 marks.				4QX10M=40M
6.	Explain the concept of Multi-Range Ammeter and Voltmeter. How are these instruments designed to measure a wide range of currents and voltages?	10 Marks	L2	CO1

or

7.	Explain the different types of errors that can occur in measurement. Provide examples of systematic and random errors, and suggest methods to minimize them.	10 Marks	L2	CO1
----	--	-------------	----	-----

8.	A resistance is measured by the voltmeter- ammeter method employing d.c. excitation and a voltmeter of very high resistance connected directly across the unknown resistance. If the voltmeter and ammeter readings are subject to maximum possible errors of 2.4% and 1% respectively, then solve for the maximum possible percentage error in the value of resistance deduced from the measurement.	10 Marks	L3	CO2
----	---	-------------	----	-----

or

9.	A PMMC voltmeter is connected across the 100 kohm resistance as shown in the figure below. Analyze the voltage waveform and magnitude of voltage displayed by the meter at the output by drawing the waveform.	10 Marks	L4	CO2
----	--	-------------	----	-----

10.	The line to line input voltage to a 3 phase 50 Hz star connected balanced AC circuit shown in figure below is 100 V and two wattmeters are connected at the input which are indicated by the circled portion in the figure given below, interpret the wattmeter readings if the phase sequence is RYB?	10 Marks	L2	CO2
-----	--	-------------	----	-----

or

<p>11.</p> <p>A Single phase wattmeter is used to measure the power supplied to an inductive load of magnitude 5 ohms and a phase of 36.86 degrees. A supply of 230 volts and 50 Hz is applied to the load. The current flowing through the load is stepped down using a 50/5 current transformer and the stepped down current is supplied to the current coil. The supply is connected directly to the potential coil.</p>	<p>10 Marks</p>	<p>L2</p>	<p>CO2</p>
--	------------------------	------------------	-------------------

<p>12.</p> <p>A PMMC voltmeter is connected across the DC and AC supply as shown in the figure. Interpret the reading that would be displayed by the meter.</p>	<p>10 Marks</p>	<p>L2</p>	<p>CO2</p>
--	------------------------	------------------	-------------------

or

<p>13.</p> <p>A periodic voltage waveform observed on an oscilloscope across a load by an engineer as shown in figure below . A permanent magnet moving coil (PMMC) voltmeter has been connected across the same load. Interpret the reading of the voltmeter in volts by stating the reason for such reading.</p>	<p>10 Marks</p>	<p>L2</p>	<p>CO2</p>
---	------------------------	------------------	-------------------



