



ROLL NO.

**PRESIDENCY UNIVERSITY, BENGALURU**  
**SCHOOL OF ENGINEERING**

Max Marks: 80

Max Time: 180 Mins

Weightage: 40 %

**ENDTERM FINAL EXAMINATION**

I Semester AY 2017-18

Course: **ECE/EEE 203 Digital Design**

21 DEC 2017

**Instructions:**

- i. Write legibly
- ii. Scientific and nonprogrammable calculators are permitted

**Part A**

[5Q x 4M= 20 Marks]

1. State the difference between flip flop and latch.
2. Explain the Race around condition which occurs in J-K flip flop.
3. Explain the role of preset and clear in sequential circuits.
4. Discuss synchronous and asynchronous circuits with example for each.
5. Explain the working of Latch as a storage element shown in fig 1.1.

 


Fig 1.1

**Part B**

[3Q x 15M= 45 Marks]

6. Explain the working of bi-directional shift register. Discuss the right shift and left shift operation
7. Design 4 bit Ring counter and draw the timing diagram.
8. Design a S-R flip flop using T flip flop
  - a. Design a characteristic table....
  - b. Design a table of excitation for -----
  - c. Design Boolean expression for the required flip-flop
  - d. Draw the circuit diagram for required flip flop using

**Part C**

[1Q x 15M= 15Marks]

9. Design a 4 bit synchronous counter with D Flip Flop.



**PRESIDENCY UNIVERSITY, BENGALURU**  
**SCHOOL OF ENGINEERING**

Max Marks: 40

Max Time: 60Min

Weightage: 20 %

**TEST 2**

I Semester AY 2017-2018

Course: **ECE/EEE 203Digital Design**

25 OCT 2017

---

**Instructions:**

- i. Write legibly
  - ii. Scientific and non programmable calculators are permitted
- 

**Part A**

(3Q x 4 M= 12 Marks)

1. Design a combinational circuit which adds two binary numbers and produces sum and carry as output.
2. Implement the following Boolean function with active low output  
 $f(x,y,z) = \sum(1,3,5,7)$   
 $f(x,y,z) = \sum(2,4,6,7)$
3. Design a combinational circuit that compares two 1-bit input.

**Part B**

(2Q x 8 M= 16 Marks)

4. Explain difference between decoder and encoder. Explain the role of enable , Construct a 5-to-32 line decoder with four 3-to-8 line and one 2-to-4 line.
5. Design a n bit adder/subtractor circuit and explain working with suitable example.

**Part C**

(1Q x 12 M= 12 Marks)

6. Design a combinational circuit that generates the 9's complement of BCD digits



# PRESIDENCY UNIVERSITY, BENGALURU

## SCHOOL OF ENGINEERING

Max Marks: 40

Max Time: 60Min

Weightage: 20 %

### TEST 1

I Semester 2017-2018

Course: ECE/EEE 203 Digital Design

20 SEPT 2017

#### Instructions:

- i. Write legibly
- ii. Scientific and non programmable calculators are permitted

#### Part A

(4Q x 3 M= 12 Marks)

1. Convert following numbers in respective form.  
a)  $(396)_{10} = ( )_2$       b)  $(27)_8 = ( )_2$       c)  $(110101)_2 = ( )_{10}$
2. Solve the following subtraction using 2's complement method.  
01100-00011
3. Solve the following expressions and simplify to minimum number of literal using Boolean rules.  
 $XY + X(WZ + WZ')$
4. For the given logic diagram as shown in fig 1 which combination of input (A,B,C) makes output (y)=1  
Draw the truth table for the same.

 


Fig 1

#### Part B

(2Q x 8 M= 16 Marks)

5. Simplify the Boolean function into a) sum-of-products from b) product of sum form using K-map  
 $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$
6. For the given function  $f = AB + AC' + C + AB'C + ABC$ 
  - a) Express f in standard SOP form
  - b) Minimize it and realize the expression using basic gates .

### Part C

(1Q x 12 M= 12 Marks)

7. For the Boolean function  $F = w'xy + wx'y + wxy$
- Obtain the truth table for the given expression
  - Draw the logic diagram using origin given expression.
  - Obtain the truth table of the function from the simplified expression and show that it is same
  - Draw the logic diagram from the simplified expression and compare the total number of gates with the diagram of part 7 (b).