



PRESIDENCY UNIVERSITY

BENGALURU

Roll No.															
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Mid - Term Examinations - March 2026

Date: 12- 03-2026

Time: 02:00pm - 03:30pm

School: SOE	Program: B.Tech		
Course Code : ECE3177	Course Name: RF Integrated Circuits & Systems		
Semester: VI	Max Marks: 50	Weightage: 25%	

CO - Levels	C01	C02	C03	C04	C05	C06
Marks	26	24				

Instructions:

- (i) Read all questions carefully and answer accordingly.
- (ii) Do not write anything on the question paper other than roll number.

Part A

Answer ALL the Questions. Each question carries 2marks.

5Q x 2M=10M

1	Briefly state the concept of resonance in the context of a series RLC circuit configuration. Identify the criterion that must be met for the circuit to achieve resonance, and remark on the circuit's impedance at the resonant frequency.	2 Marks	L1	C01
2	A series RLC circuit has $R = 20 \Omega$, $L = 0.1 \text{ H}$, and $C = 0.5 \mu\text{F}$. Calculate the resonant frequency and the Q-factor of the circuit.	2 Marks	L1	C01
3	Distinguish between lumped and distributed parameter circuits. When is lumped parameter analysis valid for transmission lines?	2 Marks	L1	C01
4	A transmission line has the following primary constants: $R = 4 \Omega/\text{km}$, $L = 3 \text{ mH}/\text{km}$, $G = 0.5 \mu\text{S}/\text{km}$, and $C = 0.03 \mu\text{F}/\text{km}$. Calculate the characteristic impedance Z_0 of the transmission line at high frequencies where R and G can be neglected.	2 Marks	L1	C02
5	What is noise figure (NF)? Express its mathematical relationship to noise factor (F).	2 Marks	L1	C02

Part B

Answer the Questions.

Total Marks 40M

6.	Distinguish between superheterodyne and direct conversion receiver architectures in RFIC, comparing their block diagrams, operational principles, selectivity, sensitivity, and noise performance.	20 Marks	L2	CO1
Or				
7.	<p>A Class-A power amplifier is designed for an RF transmitter operating at 1.8 GHz. The amplifier uses a single transistor with the following specifications and operating conditions:</p> <ul style="list-style-type: none"> • Supply voltage: $V_{DD} = 10\text{ V}$ • DC bias current: $I_{DC} = 100\text{ mA}$ • Load resistance: $R_L = 100\ \Omega$ • Output power at 1-dB compression point: $P_1\text{ dB} = 20\text{ dBm}$ • The amplifier delivers a sinusoidal RF output signal with peak voltage swing of 3 V <p>Calculate:</p> <p>(a) The DC power consumed by the amplifier (P_{DC}).</p> <p>(b) The output RF power delivered to the load (P_{out}).</p> <p>(c) The power-added efficiency (PAE) of the amplifier, assuming input power $P_{in} = 10\text{ mW}$.</p> <p>(d) The drain efficiency (η) of the amplifier.</p>	20 Marks	L2	CO1

8.	a.	What is the typical noise figure range for a low-noise amplifier (LNA) in RF applications, and why is minimizing noise figure important in receiver design?	10 Marks	L2	CO2
	b.	Express the noise figure formula for a cascaded system of two stages using Friis formula.	10 Marks	L3	CO2
Or					
9.	a.	How does the noise figure of an amplifier change with temperature? State the standard reference temperature used for noise figure measurements.	10 Marks	L2	CO2
	b.	What is phase noise in RF circuits? Discuss its impact on receiver sensitivity and specify the key performance metric used to quantify phase noise in local oscillators.	10 Marks	L3	CO2