



PRESIDENCY UNIVERSITY

BENGALURU

Roll No.														
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--

End - Term Examinations – May / June 2026

Date: 20- 05-2026

Time:01:00pm – 04:00pm

School: SOE	Program: B.Tech	
Course Code: ECE3050	Course Name: Design for Testability (DFT)	
Semester: VI	Max Marks: 100	Weightage: 50%

CO - Levels	C01	C02	C03	C04	C05	C06
Marks	20	16	16	8	20	20

Instructions:

- (i) Read all questions carefully and answer accordingly.
- (ii) Do not write anything on the question paper other than roll number.

Part A

Answer ALL the Questions. Each question carries 2marks.

10Q x 2M=20M

1.	Probability-based controllability extends traditional system control theory by accounting for stochastic behaviors, component failures, or uncertain environmental conditions. What is the boundary condition for controllability and observability based on Probability approach?	2 Marks	L1	C02
2.	Scan architecture is a Design for Testability (DFT) technique that converts internal sequential elements (flip-flops) into a shift registers. What are different IOs in scan architecture?	2 Marks	L1	C03
3.	SCOAP (Sandia Controllability & Observability Analysis Program) is a testability analysis technique in Design for Testability (DFT) that quantifies how easy or hard it is to control and observe internal digital circuit nodes. Compute SCOAP and probability-based testability measures of a 3 input AND Gate?	2 Marks	L1	C02
4.	High controllability simplifies testing, reducing the need for extensive test vectors and increasing fault coverage Define controllability?	2 Marks	L1	C02

5.	A scan cell in Design-for-Test (DFT) is a modified flip-flop (typically a Muxed-D type) that replaces standard flops to enhance controllability and observability. Draw a neat sketch of Muxed D scan cell?	2 Marks	L1	C03
6.	Scan cell primarily refers to a specialized VLSI flip-flop used in circuit testing. What are different scan cell designs?	2 Marks	L1	C03
7.	Faults often causing devices to stop working, overheat, or enter protect mode. Common causes include thermal overstress, excessive voltage/current, or physical damage. Define open and short faults?	2 Marks	L1	C04
8.	For a circuit of n fault sites and k types of faults, how many single faults will be present?	2 Marks	L1	C04
9.	Defect levels define the quality threshold of products, typically measured as the percentage of faulty items or defects per million (DPM). Write the equation for defect level?	2 Marks	L1	C04
10.	Faults in Design for Testability (DFT) are logical representations of physical manufacturing defects, Define bridging fault?	2 Marks	L1	C04



Part B


Answer the Questions.

Total Marks 80M


11.	a.	At the switch level, a transistor can be stuck open or stuck short. These fault models cannot accurately reflect the behaviour of faults in CMOS logic circuits because of multiple transistors used. Illustrate the concept of above stuck faults in 2 input CMOS NAND gate with the help of truth table and explanation?	10 Marks	L2	C01
	b.	The VLSI development process is a structured, multi-stage methodology transforming a conceptual idea into a physical silicon chip, involving system specifications, logic design, functional verification, physical design (layout), and fabrication. Explain different levels of abstraction in VLSI design verification?	10 Marks	L3	C01
Or					
12.	a.	The number of failures in 10 power 9 hours is a unit (abbreviated FITS) that is often used in reliability calculations. There is a system with 200 components where each component has a failure rate of 1000 FITS, yield is 60% with fault coverage as 20% and system availability as 99.999%. Calculate the overall failure rate, MTBF, MTTR, repair rate, and defect level, for this system with necessary formulas?	10 Marks	L2	C01
	b.	Bridging faults are those faults that involve a short between two signal lines in the digital circuit. The logic behaviour of a short defect between signal lines is commonly represented by the	10 Marks	L3	C01

		bridge fault model. Illustrate the concept of above faults with an example using truth table and explanation?			
--	--	---	--	--	--

  13.	a.	Scan design in DFT is a technique that replaces standard flip-flops with scan-enabled cells, connecting them into chains to boost controllability and observability. Explain about Clocked Scan Cell design and operation with suitable diagrams and waveforms?	10 Marks	L2	C03
	b.	What are the SCOAP Combinational Controllability Calculation Rules for 1-Controllability (Primary Input, Output, Branch) of AND, OR, NOT gates. Calculate the SCOAP based Combinational Controllability and Observability measures for the following circuit? 	10 Marks	L3	C02
Or					
14.	a.	Explain about Partial Scan circuit and test operation of scan architecture with neat sketches?	10 Marks	L2	C03
	b.	What are the Probability based Controllability Calculation Rules for 1-Controllability (Primary Input, Output, Branch) of AND, OR, NOT gates. Calculate the Probability based Combinational Controllability and Observability measures for the following circuit? 	10 Marks	L3	C02

 15.	a.	A) Explain the steps in D algorithm? Generate the test vector for SA0 fault on the line f as shown in figure using table?  B) Draw the D intersection table of above D Algorithm?	20 Marks	L2	C05
-----	----	---	----------	----	-----

Or

 16.	a.	Find Test vectors for SA-0 Fault at x3 input for the following function using Boolean difference method $((x_1 + x_2) \cdot \overline{x_3}) + x_3 x_4$	10 Marks	L2	C05
	b.	Explain Transistor faults with an example and for the Given circuit if g is having SA1 fault then find the test vector using path sensitization technique? 	10 Marks	L2	C05

17.	a.	Explain BIST with neat sketch? Explain the Logic BIST techniques in detail?	10 Marks	L2	C06
	b.	Write a detail description about LFSR types and properties with a neat sketch? Generate the test sequence for both types using an example?	10 Marks	L2	C06
Or					
18.	a.	How test pattern generation is constructed in BIST? Explain in detail with an example	10 Marks	L2	C06
	b.	Write about serial signature analysis with a neat sketch and generate the signature table for faulty and fault free circuit?	10 Marks	L2	C06