

Roll No																			
---------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



**PRESIDENCY UNIVERSITY
BENGALURU**

**SCHOOL OF ENGINEERING
END TERM EXAMINATION - JAN 2023**

Semester : Semester V - 2020

Course Code : ECE3008

Course Name : Sem V - ECE3008 - VLSI Design

Program : B.Tech. Electronics and Communication Engineering

Date : 11-JAN-2023

Time : 9.30AM - 12.30PM

Max Marks : 100

Weightage : 50%

Instructions:

- (i) Read all questions carefully and answer accordingly.
- (ii) Question paper consists of 3 parts.
- (iii) Scientific and non-programmable calculator are permitted.

PART A

ANSWER ALL THE FIVE QUESTIONSQ

5 X 2 = 10M


1. There are various operators available in verilog HDL like Logical operator, Boolean Logical operator, Reduction Logical operator, Relational operators. Consider the following code $X = 1010$ and perform reduction AND operation on it.
(CO1) [Knowledge]
2. The logic element like an inverter reverses the applied input signal. In digital logic circuits, binary arithmetic & switching or logic function's mathematical manipulation are best performed through the symbols 0 & 1. Draw a Static CMOS Circuit for an "INVERTER".
(CO3) [Knowledge]
3. Transmission gates are parallel combination of pmos and nmos transistor with the gates connected to a complementary input. complete the following sentences.
When $C = \text{___}$ n and p device ____, $V_{in} = 0$ or 1, $V_o = \text{"Z"}$ where „Z“ is high impedance.
When $C = \text{___}$ n and p device ____, $V_{in} = 0$ or 1, $V_o = 0$ or 1 ,
(CO3) [Knowledge]
4. The transfer characteristic relates drain current (I_d) response to the input gate-source driving voltage (V_{gs}) for a MOSFET . Draw the Graph of V_{ds} Vs I_d
Identify the various regions of operation of a N-MOSFET.
(CO2) [Knowledge]
5. There are main three types of scaling stated as general scaling, constant field and constant voltage scaling. In general scaling state the scaling factor for idss.
(CO2) [Knowledge]

PART B

ANSWER ALL THE TWO QUESTIONS

2 X 15 = 30M

6. Stick diagrams are helpful in sketching an initial layout of a CMOS-based circuit. Consider the following stick diagram and do the following:
- Draw the CMOS circuit implementation by showing both Pull-up and Pull-down networks.
 - Identify the number of valid Euler's Paths and list them.

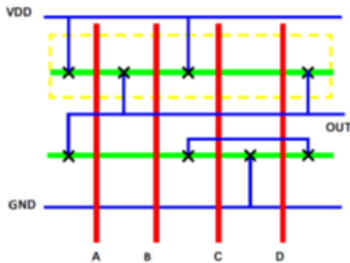

(CO3) [Comprehension]

7. A CMOS circuit consists of a pull-up network and a pull-down network. Draw the CMOS transistor network implementation of the Boolean expression: $F = \overline{DE} + C(A + B)$

(CO3) [Comprehension]

PART C

ANSWER ALL THE THREE QUESTIONS

3 X 20 = 60M

8. A game is designed where inputs are chosen in decimal numbers varying from 0 to 7 but outputs are obtained in binary form. A user starts playing with this game designed such that if he presses button 17 the output is obtained in binary form as 111, similarly for 15 as 101 and so on. If the user presses two buttons at a time then the button with higher decimal notation would be chosen. Design the circuit for the defined scenario using Behavioural modelling style in Verilog and write its Truth Table along with Expected Output Waveform.

(CO1) [Application]

9. The drain characteristics of a MOSFET are drawn between the drain current I_D and the drain source voltage V_{DS} . V_{GS} also plays an important role to depict the region of operation and switch on the transistor. Compute the unknown values for the following numerical based questions.
- The gate to source voltage of a nmos working with $V_t = 0.4$ V is 0.9 V, while region of operation here is saturation region. The value of drain current is 1mA. Compute the value of I_D when $V_{GS} = 1.4$ V.
 - The drain of NMOS is shorted to gate. $V_t = 1$ V, if $I_D = 1$ milli-amps at $v_{gs} = 2$ V, find the value of I_D at $V_{GS} = 3$ V.

(CO2) [Application]

10. Digital inverter quality is often measured using the Voltage Transfer Curve (VTC), which is a plot of input vs. output voltage. From such a graph, device parameters including noise tolerance, gain, and operating logic-levels can be obtained. Illustrate all the five cases pertaining to the VTC curve. Include the operating region for both transistors in the cases and explain it for values: $V_{th} = 0.4$ V and $V_{DD} = 5$ V.

(CO3) [Application]
