

Roll																			
No.																			



**PRESIDENCY UNIVERSITY
BENGALURU**

SCHOOL OF ENGINEERING

MAKEUP EXAMINATION – JAN 2023

Course Code: ECE 2007

Date: 23-JAN-2023

Course Name: Digital Design

Time: 1:00PM to 4:00 PM

Programme : B. Tech

Max Marks: 100

Weightage: 50%

Instructions:

- (i) **Read Questions carefully and answer accordingly**
- (ii) **Scientific and Non- programmable calculators are permitted**
- (iii) **This Examination mode is OFFLINE**

PART A (Memory Recall Questions)

Answer all the questions. Each question carries TWO Marks.

[15Q x 2M = 30M]

1. NAND & NOR GATES are called as _____ **(CO.1) [B. Level: Knowledge]**
2. There are 16 input combinations in a digital system, how many minimum variables are required to frame a Boolean Function ? **(CO.1) [B. Level: Knowledge]**
3. Karnaugh map is used to simplify Boolean expression. How many cells are present in 4 variable k-map. Each product term of a group, $w'.x.y'z$ and $wx.y,z$ represents the _____ in that group **(CO.1) [B. Level: Knowledge]**
4. In two input NAND gate one of the input goes to low level, then the output is _____ **(CO.1) [B. Level: Knowledge]**
5. An Encoder is a combinational logic circuit; it encodes certain set of inputs to outputs. In 2^N : N encoder the OUTPUT has _____ bit binary form. **(C.O.No.3) [Knowledge]**
6. An adder is a combinational logic circuit whose output are sum and carry. If two numbers, $(6)_{10}$ and $(7)_{10}$ are added using a full adder. At LSB position of both the numbers, _____ will be the sum ---- and _____ will be the carry. **(C.O.No.2) [Knowledge]**
7. A Half adder is an arithmetic circuit that adds two binary digits. It uses _____ gate & _____ gate. Its output are SUM & CARRY **(C.O.No.2) [Knowledge]**
8. Multiplexer (MUX) is a Combinational logic circuit having single output line and many input lines. Four variable Boolean function can be implemented using (with the minimal select lines)MUX. **(C.O.No.3) [Knowledge]**
9. The outputs of a comparator irrespective of number of bits are _____, _____ and _____.
10. Any number can be represented in various base systems. Find the equivalent of $(12)_{10}$ in $(\quad)_2$, $(\quad)_8$, $(\quad)_{10}$ and $(\quad)_{16}$? **(CO.1) [B. Level: Knowledge]**
11. A J-K flip flop is designed to overcome the shortcomings of S-R latch. What is the major difference between S-R latch and S-R Flipflop? How S-R Flipflop can be modified to work as a D-Flipflop. **(C.O.No.3) [Knowledge]**

- 12 Multiplexer are combinational circuit which has certain input and output lines. In addition to this, other input signals are present in MUX design called select lines. A 16:1 MUX has _____ inputs, _____ output & _____ selection lines . **(C.O.No.2)**
[Knowledge]
- 13 For designing a 4 bit Asynchronous counter how many JK flipflop are required? Which input combinations it produces no change state? **(C.O.No.3) [Knowledge]**
- 14 T –flip flop is modified version of -----Flip flop , In T-flip flop ,for what input combinations it produces no change state? **(C.O.No.3) [Knowledge]**
- 15 Digital circuits can be broadly classified as Combinational circuits, and Sequential circuits. In a combinational circuit, the output depends on **(C.O.No.3) [Knowledge]**

PART B (Thought Provoking Questions)

Answer any 4 Questions. Each Question carries 10 Marks. [4Q x 10M = 40M]

- 16 .Roy and his friends are interested to design a block that has 16 input lines and 1 output and that block is named as Multiplexer that performs reverse operation of a De-Multiplexer. Help them to build the block but they have only 2:1 MUX. Hence, implement 16:1 MUX using 2:1 MUX.
[CO2 B. Level: Comprehension]
- 17.Mr JOY wants to implement a warning buzzer when the following conditions apply:
- Switches A, B, C are on.
 - Switches A and B are on but switch C is off
 - Switches A and C are on but switch B is off.
 - Switches C and B are on but switch A is off.
- Draw a truth table for this situation and obtain a Boolean expression for it.Minimize this expression and draw a logic diagram using NAND GATES.
[CO2 B. Level: Comprehension]
18. Find the Boolean expression in sum of product (SOP) from the given truth table and simplify the expression using K Map.

Inputs			Outputs
A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

- [CO2 B. Level: Comprehension]**
- a) Design and implement the simplified logic using LOGICAL GATES.
- b) Design and implement the simplified logic using 4:1 MUX **[CO2 B. Level: Comprehension]**

19. A comparator is a device that compares two bits, voltage or currents and outputs a digital signal indicating which is larger. Design a **1-Bit comparator** with the help of truth table and obtain the logical expression for each case with the help of simplification method (K-map).
[CO2 B. Level: Comprehension]
-

PART C (Problem Solving Questions)

Answer any 2 the Questions. Each Question carries 15 Marks.

[2Q x 15M = 30M]

20. You can create a 3-input, 3-output circuit that maps one state in the *count* sequence to the next. Design synchronous 3 bit up counter using T flipflop.

- Write excitation table of Flip Flop
- Draw the state transition diagram and circuit state table.
- Find a simplified equation using k map.
- Create a circuit diagram

(C.O.No. 3) [Application]

21. In Boolean algebra, circuit minimization is the problem of obtaining the smallest logic circuit that represents a given Boolean function or truth table. Mr Joel is provided with Boolean function

$$F = \sum m(0,1,4,7,9,13,15)$$

- Write whether the below expression is an SOP or POS expression and what is the full-form? Write whether the below expression is a min-term or max-term expression? How many variable K-map we need to simplify the below expression? Draw the K-map and simplify the above expression by showing all the steps.
- Implement the simplified expression obtained in Part (b) using basic gates.
- Implement the simplified expression obtained in Part (b) using NAND gates. .

(C.O.No. 2) [Application]

22. A sequential circuit refers to a special type of circuit where the outputs depend on a combination of both the present inputs as well as the previous outputs.

- Discuss the comparison between Synchronous and Asynchronous circuits.
- Design a 3-bit Asynchronous up-counter, how many flip flops required and mention the number of states using state diagram.

(C.O.No. 2) [Application]