

Roll No																			
---------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



**PRESIDENCY UNIVERSITY
BENGALURU**

SET B

**SCHOOL OF ENGINEERING
END TERM EXAMINATION - JAN 2024**

Semester : Semester III - 2022

Course Code : EEE2009

Course Name : Analog Electronics Circuits

Program : B.Tech.

Date : 08-JAN-2024

Time : 9:30AM - 12:30 PM

Max Marks : 100

Weightage : 50%

Instructions:

- (i) Read all questions carefully and answer accordingly.
 - (ii) Question paper consists of 3 parts.
 - (iii) Scientific and non-programmable calculator are permitted.
 - (iv) Do not write any information on the question paper other than Roll Number.
-

PART A

ANSWER ALL THE QUESTIONS

5 X 2M = 10M

1. In a common base connection, $\alpha = 0.95$. The voltage drop across $2\text{ k}\Omega$ resistance which is connected in the collector is 2V . Find the base current.
(CO1) [Knowledge]
2. In a common base connection, $I_E = 1\text{mA}$, $I_C = 0.95\text{mA}$. Calculate the value of I_B .
(CO1) [Knowledge]
3. Explain with a circuit of Series Negative Clipper.
(CO2) [Knowledge]
4. What is clamper and its application?
(CO2) [Knowledge]
5. Find the value of β if (i) $\alpha = 0.9$ (ii) $\alpha = 0$.
(CO3) [Knowledge]

PART B

ANSWER ALL THE QUESTIONS

5 X 10M = 50M

6. Calculate the V_{dc} , $V_r(\text{rms})$ through a $1\text{K}\Omega$ load connected to a half-wave rectifier circuit shown in fig
(CO1, CO3) [Comprehension]

7. To achieve maximum voltage gain, which is the most suitable transistor configuration for cascading? and brief the same.
(CO3,CO1) [Comprehension]
8. Design a Colpitts oscillator using the data given below:
A 1 mH inductor is available. Choose the capacitor values in a Colpitts oscillator so that $f = 1$ MHz and $m_v = 0.25$.
(CO3,CO1) [Comprehension]
9. Prakash conducted experiment in a laboratory and Produce a oscillation using Colpitts Oscillator.Discuss the operation of Colpitts Oscillator.
(CO4,CO3,CO1) [Comprehension]
10. A 1 pF capacitor is available. Choose the inductor values in a Hartley oscillator so that $f = 1$ MHz and $m_v = 0.2$.
(CO5,CO3,CO1) [Comprehension]

PART C

ANSWER ALL THE QUESTIONS

2 X 20M = 40M

11. A JFET in Fig. 4 has values of $V_{GS}(\text{off}) = -8\text{V}$ and $I_{DSS} = 16\text{ mA}$. Determine the values of V_{GS} , I_D and V_{DS} for the circuit
(CO2,CO3) [Application]
12. In an n-channel JFET biased by potential divider method, it is desired to set the operating point at $I_D = 2.5\text{ mA}$ and $V_{DS} = 8\text{V}$. If $V_{DD} = 30\text{ V}$, $R_1 = 1\text{ M}\Omega$ and $R_2 = 500\text{ k}\Omega$, find the value of R_S . The parameters of JFET are $I_{DSS} = 10\text{ mA}$ and $V_{GS}(\text{off}) = -5\text{ V}$
(CO3,CO4) [Application]