

| | | | | | | | | | | | | | | | | | | | |
|---------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| Roll No | | | | | | | | | | | | | | | | | | | |
|---------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|



**PRESIDENCY UNIVERSITY
BENGALURU**

**SCHOOL OF ENGINEERING
MID TERM EXAMINATION - OCT 2023**

Semester : Semester III - 2022

Course Code : ECE2007

Course Name : Sem III - ECE2007 - Digital Design

Program : B. TECH

Date : 31-OCT-2023

Time : 11:30AM - 1:00PM

Max Marks : 50

Weightage : 25%

Instructions:

- (i) Read all questions carefully and answer accordingly.
- (ii) Question paper consists of 3 parts.
- (iii) Scientific and non-programmable calculator are permitted.
- (iv) Do not write any information on the question paper other than Roll Number.

PART A

ANSWER ALL THE QUESTIONS

(5 X 2 = 10M)

1. There are 8 input combinations in the truth table of digital system. State the number of input variables for framing a standard form Boolean expressions? Also draw K map template for the same
(CO1) [Knowledge]
2. The Boolean Algebra specifies various laws for simplification of logic expression the Boolean Law $A+A'B=$ _____.
(CO1) [Knowledge]
3. Any number can be represented in various base systems. Find the equivalent of $(12)_{10}$ in $(\quad)_2$, $(\quad)_8$, $(\quad)_{16}$ and $(\quad)_{BCD}$?
(CO1) [Knowledge]
4. A comparator is a device that compares two bits, voltage or currents and outputs a digital signal indicating which is larger. Design a 1-Bit comparator with the help of truth table and obtain the logical expression for each case with the help of simplification method (K-map).
 - i) Implement Using Logical Gates
 - ii) Using NAND gates.
(CO2) [Knowledge]
5. A Half Adder is an arithmetic circuit that adds two binary digits. It uses _____ gate & _____ gate for computing SUM and CARRY output respectively.
(CO2) [Knowledge]

PART B

ANSWER ALL THE QUESTIONS

(2 X 10 = 20M)

6. A combinational logic circuit has 4 inputs, the output will be high only when the majority of the inputs are high. Draw a truth table for this situation and obtain a Boolean expression for it. Minimize this expression and draw a logic diagram using basic gates and NAND gates only
(CO1) [Comprehension]
7. The input to combinational logic circuit is a 4 bit binary number. Derive the truth table and implement using basic gates and NAND gates only when Output $y=1$ if the input binary number is 5 or less than 5.
(CO2) [Comprehension]

PART C

ANSWER THE FOLLOWING QUESTION

(1 X 20 = 20M)

8. Implement a warning buzzer when the following conditions apply:
- Switches A, B and C are off.
 - Switches A and B are off but switch C is on.
 - Switches A and C are off but switch B is on.
 - Switches C and B are off but switch A is on.
- Draw a truth table for the complement of this situation and obtain a Boolean expression for it. Minimize this expression and draw a logic diagram using a) basic gates and b) NAND gates only.
(CO2) [Application]