



Roll No																			
---------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

PRESIDENCY UNIVERSITY BENGALURU

Department of Research & Development

Mid - Term Examinations - August 2024

Odd Semester: Ph.D. Course Work

Course Code: EEE811

Course Name: EV Battery Charging Technology

Department: SoE/EEE

Date: 12/08/2024

Time: 9:30am – 11:00am

Max Marks: 50

Weightage: 25%

Instructions:

- (i) Read the all questions carefully and answer accordingly.
 - (ii) Do not write any matter on the question paper other than roll number.
-

PART A (THOUGHT PROVOKING)

Answer all the Questions. Each question carries 5 marks.

(4Qx 5M= 20M)

1. Draw and Explain Basic charging Block Diagram of Charger.
(CO:1 Comprehension)
2. Explain the fundamental differences between AC and DC charging in electric vehicles. Discuss how the power conversion process occurs in each case and the implications for charging infrastructure.
(CO:1 Comprehension)
3. What is DAB Topology? Discuss its Real-Life Applications.
(CO:2 BL:1Comprehension)
4. What is the principle of operation of a Dual Active Bridge (DAB) converter?
(CO:2 BL:1Comprehension)

PART B (PROBLEM SOLVING)

Answer all the Questions. Each question carries 10 marks.

(3Qx 10M= 30M)

5. Consider an EV with a 85 kWh battery that has been used for 5 years, resulting in a 10% capacity degradation. The vehicle is being charged using a Level 2 charger that supplies 11 kW of power. Due to aging, the battery's internal resistance has increased, leading to a reduced charging efficiency of 80%. The battery is currently at 15% SoC, and you aim to charge it to 100%.
 - a) Calculate the degraded battery capacity.

- b) Determine the actual energy that must be drawn from the grid to charge the battery from 15% to 100% SoC.
- c) Estimate the total charging time, considering the efficiency loss.

(CO:1 BL:Application)

6. Consider an EV with a 90 kWh battery capable of accepting a maximum charging power of 150 kW. The charging rate, however, is not constant. The charging profile is as follows:
- From 10% to 50% SoC, the charger provides the maximum 150 kW.
 - From 50% to 80% SoC, the charging power decreases linearly to 60 kW.
 - Beyond 80% SoC, the power decreases further to 30 kW and remains constant until 90% SoC.

The battery temperature starts at 30°C and increases by 1°C for every 10 minutes of charging. When the battery temperature reaches 50°C, the charging power must be reduced by 10% to prevent overheating. The ambient temperature is constant at 25°C.

- a) Develop a piecewise function to model the charging power as a function of SoC and time.
- b) Calculate the total energy required to charge the battery from 10% to 90% SoC.
- c) Determine the total charging time considering the thermal constraints. Integrate the charging power function over time to obtain the total charging duration.
- d) Discuss how thermal management strategies impact the overall charging time and battery lifespan.

(CO:1 BL:3 Application)

7. A 400W LLC resonant converter operates with an input voltage V_{in} of 400V and an output voltage V_{out} of 24V. The switching frequency f_s is 100kHz, and the resonant tank consists of the following parameters:

Resonant inductor L_r : 100 μ H, Resonant capacitor C_r : 20nF, Magnetizing inductance L_m : 400 μ H

- a) Calculate the resonant frequency f_0 of the LLC converter.
- b) Determine the characteristic impedance Z_r of the resonant tank.
- c) Find the quality factor Q of the resonant circuit.
- d) Calculate the maximum gain of the converter.

(CO:2 BL:3 Application)